

Introduction to AC Circuits

Meet Soni

Assistant Professor
Electrical Engineering

Content

- | | |
|-----------------------------------|---|
| 1. Introduction to AC circuit | 1 |
| 2. Significance of AC Supply | 2 |
| 3. Sinusoidal Voltage and Current | 3 |
| 4. Mathematical Representation | 4 |
| 5. Graphical Representation | 5 |

Introduction to AC Circuit

- An AC (Alternating Current) circuit is an electrical circuit powered by an alternating source, where the current changes its direction and magnitude periodically. Unlike DC circuits, AC circuits include reactance due to capacitors and inductors, which affect current flow.
- **Key characteristics of AC circuits:**
 - Voltage and current vary sinusoidally.
 - Includes resistance (R), inductance (L), and capacitance (C).
 - Frequency and phase angle are essential parameters.

Significance of AC Supply

- Alternating Current (AC) is the standard form of electricity delivered to homes and industries.
- **Highlighting Points:**
 - Efficient Long-Distance Transmission
 - Transformers Can Easily Step Up or Down Voltage
 - Widely Available and Cost-Effective
 - Suitable for Motors, Appliances, and Lighting
- **Note:** AC supply is preferred over DC for power distribution due to its ability to be transformed and transmitted over long distances with minimal losses.

Sinusoidal Voltages and Currents

- In AC systems, sinusoidal waveforms are most commonly used because of their smooth, repetitive nature and ease of analysis.
- A sinusoidal voltage or current can be described using amplitude, frequency, angular frequency, and phase angle.
- Standard form:
 - Voltage: $v(t) = V_m \sin(\omega t + \phi)$
 - Current: $i(t) = I_m \sin(\omega t + \theta)$
- Where:
 - V_m, I_m : Maximum (peak) values
 - ω : Angular frequency = $2\pi f$
 - ϕ, θ : Phase angles in radians
 - f : Frequency in Hz
 - t : Time in seconds

Mathematical Representation

- Sinusoidal voltage and current waveforms follow a predictable mathematical pattern:

Highlighting Points:

- Instantaneous value: Value of voltage or current at any instant.
- Peak value: Maximum amplitude of waveform.
- RMS value: $V_{rms} = V_m / \sqrt{2}$, $I_{rms} = I_m / \sqrt{2}$
- Time period (T): $T = 1/f$
- These parameters help in analyzing real-time behavior of AC signals in electrical circuits.

Graphical Representation

- The sine wave is a graphical representation of alternating current and voltage.

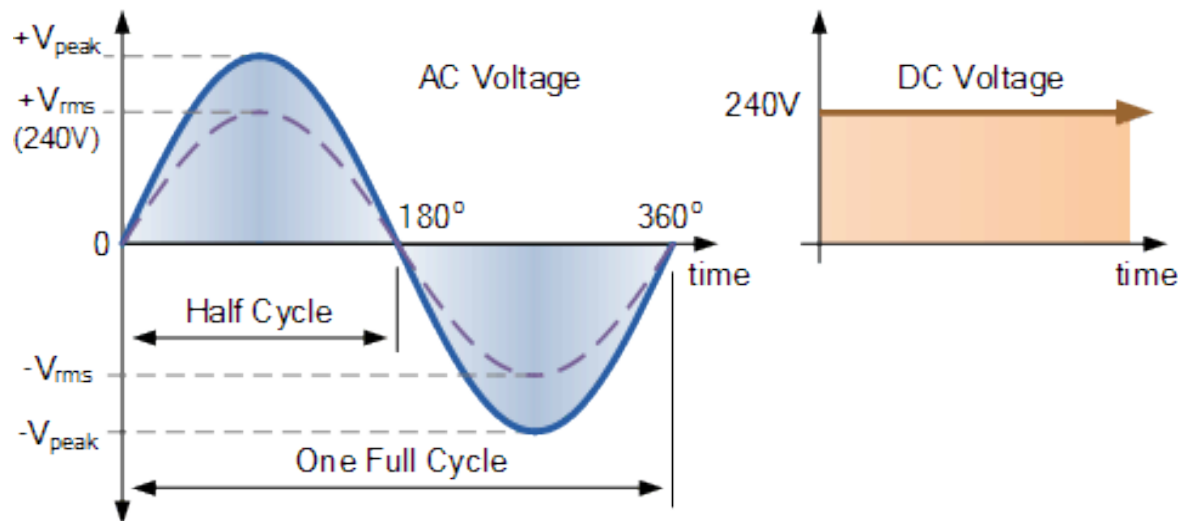


Figure 1: Standard sinusoidal waveform of voltage

Parul[®]
University

NAAC
GRADE **A++**



<https://paruluniversity.ac.in/>



Sinusoidal Quantities and Phasor Representation

Meet Soni


Assistant Professor
Electrical Engineering

Content

1. Instantaneous Value	1
2. Peak (Maximum) Value	2
3. Average Value	3
4. R.M.S. Value	4
5. Frequency, Cycle, and Period	5
6. Peak Factor and Form Factor	6
7. Phase Difference	7
8. Lagging, Leading, and In-Phase Quantities	8
9. Phasor Representation	9

Instantaneous Value

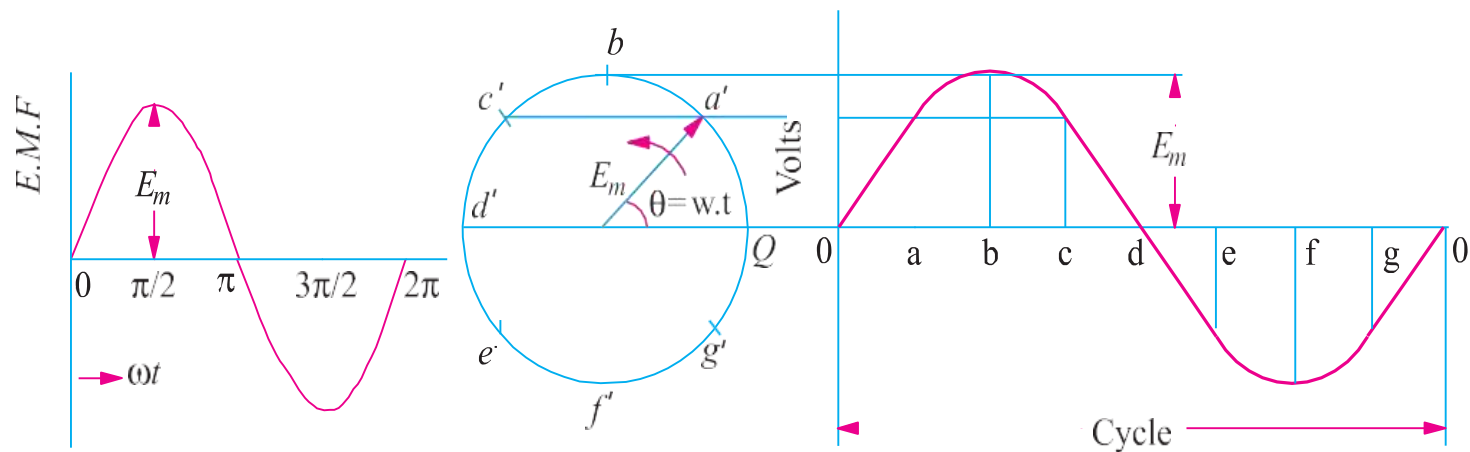- The instantaneous value of a sinusoidal quantity refers to its magnitude at a particular instant of time.
- Mathematical expression: $v(t) = V_m \sin(\omega t + \phi)$



Peak (Maximum) Value

- The peak value is the maximum value (positive or negative) reached by a waveform during one cycle.
- Highlighting Points:
 - Denoted by: V_m or I_m
 - Represents the amplitude of the wave
 - Occurs once every half cycle

Average Value

- The average value of a pure sinusoidal wave over a full cycle is zero.
- However, for practical calculations, average value is taken over one-half cycle.
- Average Value Formula:

$$V_{avg} = 2V_m / \pi$$

$$I_{avg} = 2I_m / \pi$$

R.M.S. Value

- R.M.S. (Root Mean Square) value represents the effective or equivalent DC value of an AC quantity.

- Formula:

$$V_{rms} = V_m / \sqrt{2}$$

$$I_{rms} = I_m / \sqrt{2}$$

- Highlighting Points:
- Used in power calculations
- Most commonly used value in AC analysis

Frequency, Cycle, and Period


- Cycle : One complete set of positive and negative values of alternating quantity is known as cycle
- Time Period: The time taken by an alternating quantity to complete one cycle is called its time period T . For example, a 50-Hz alternating current has a time period of $1/50$ second.
- Frequency : The number of cycles/second is called the frequency of the alternating quantity. Its unit is hertz (Hz).

Peak Factor and Form Factor

- Peak Factor = Peak Value/RMS Value
 $=V_m/V_{rms} \approx 1.414$
- Form Factor = RMS Value/Average Value
 $=V_{rms}/V_{avg} \approx 1.11$
- Highlighting Points:
 - Used in waveform comparison
 - Standard values for pure sine wave


Phase Difference

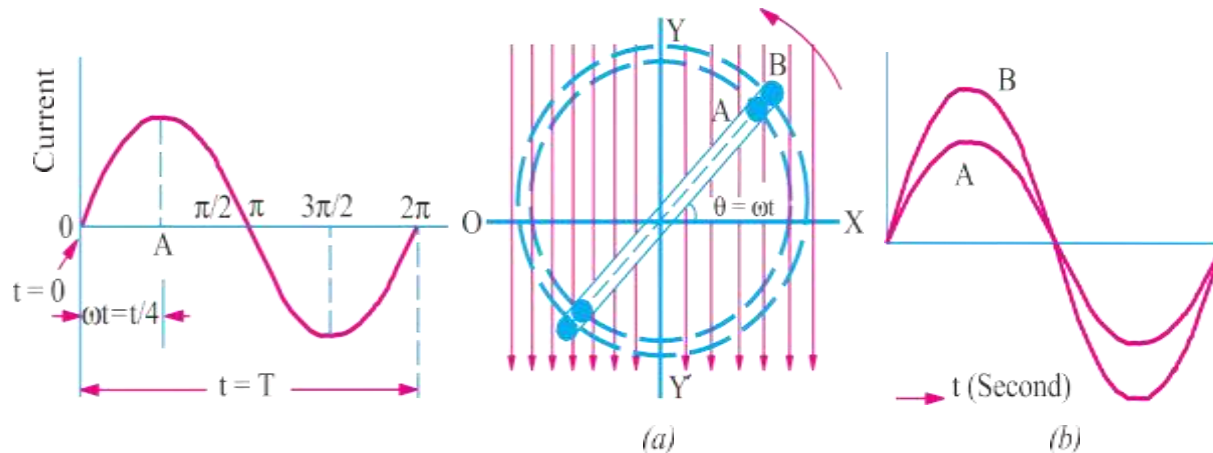- Phase difference is the angular displacement between two sinusoidal waveforms of the same frequency.



Phase Difference

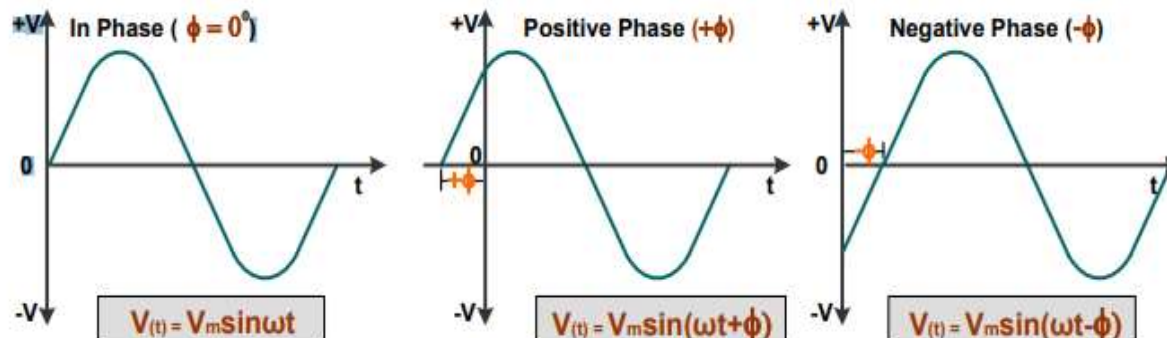
- Leading phase difference: A quantity which attains its zero or positive maximum value before the compared to the other quantity.
- Lagging phase difference: A quantity which attains its zero or positive maximum value after the other quantity.
- In-Phase: Voltage and current reach maxima/minima at the same time



Phasor Representation

- A phasor is a rotating vector representing a sinusoidal function with constant amplitude and frequency.
- Used to simplify the analysis of sinusoidal waveforms in AC circuits.
- Phasor Notation:
 - $V = V_m \angle \phi$
 - $I = I_m \angle \theta$
- Highlighting Points:
 - Easier to apply Ohm's Law and KVL/KCL in AC
 - Visualizes phase relationships clearly

Phasor Representation

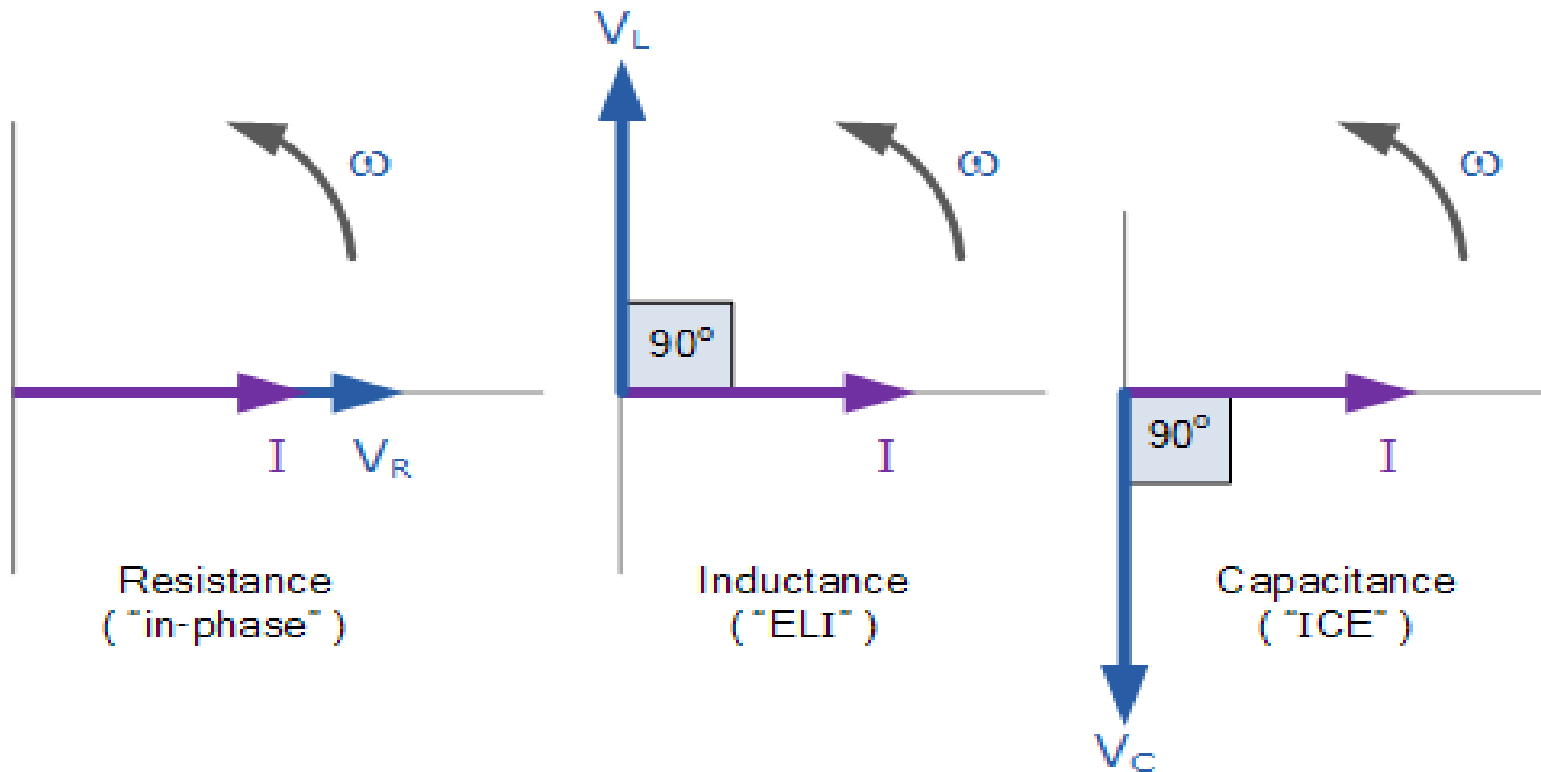

Parul[®]
University

NAAC
GRADE **A++**



<https://paruluniversity.ac.in/>



Rectangular and Polar Representation of Phasors, Examples Based on Theory

Meet Soni

Assistant Professor
Electrical Engineering

Content

1. Introduction to phasor representation	1
2. Rectangular form of phasor	2
3. Polar form of phasor	3
4. Conversion: Rectangular to Polar	4
5. Conversion: Polar to Rectangular	5
6. Example 1: Conversion of a Phasor	6
7. Example 2: AC Circuit Using Polar Representation	7
8. Graphical Representation of Phasors	8

Introduction to Phasor Representation

- A phasor is a complex number representing a sinusoidal function of time in the frequency domain. It simplifies analysis of AC circuits by converting differential equations into algebraic equations.
- Highlighting Points:
 - Phasors contain both magnitude and phase angle
 - Used in steady-state sinusoidal analysis

Rectangular Form of Phasor

- In Rectangular form, a phasor is expressed as:

$$A = x + jy$$

Where:

x : Real part (horizontal axis)

y : Imaginary part (vertical axis)

$$j = \sqrt{-1}$$

- Highlighting Points:
 - Useful in phasor addition/subtraction
 - Represents phasors on the complex plane

Polar Form of Phasor

- In Polar form, a phasor is represented as: $A = |A| \angle \theta$
- Where:
 - $|A|$: Magnitude of the phasor
 - θ : Phase angle (degrees or radians)
- Highlighting Points:
 - Preferred for phasor multiplication/division
 - Provides clear view of phase relationship

Conversion: Rectangular to Polar

To convert $A=x+jy$ to polar form:

- Magnitude: $|A|=\sqrt{x^2+y^2}$
- Angle: $\theta=\tan^{-1}(y/x)$

Highlighting Points:

- Make sure to adjust angle according to quadrant

Conversion: Polar to Rectangular

To convert $A = |A| \angle \theta$ to rectangular form:

- Real part: $x = |A| \cos(\theta)$
- Imaginary part: $y = |A| \sin(\theta)$

Highlighting Points:

- Angle must be in radians if using a calculator
- Helps in using phasors in matrix or loop equations

Example 1 – Conversion of a Phasor

Given: $A=6+j8$

- Magnitude: $|A|=\sqrt{36 + 64}$
 $=10$
- Angle: $\theta=\tan^{-1}(8/6)$
 $=53.13^\circ$
- Polar Form: $A=10\angle 53.13^\circ$
 $=10\angle 53.13^\circ$

Highlighting Points:

- Accurate angle is important in power factor analysis

Parul[®]
University

NAAC
GRADE **A++**



<https://paruluniversity.ac.in/>



Analysis with phasor diagram of Purely Resistive Load

Meet Soni

Assistant Professor
Electrical Engineering

Content

1.Introduction to AC and Resistive Loads	3
2.Characteristics of Purely Resistive Load	4
3.Voltage and Current Relationship	5
4.Phase Representation	6
5.Waveforms of Voltage and Current	7
6.Power in Pure Resistive Load	8
7.Key Points / Summary	9

Introduction to AC and Resistive Load

- Alternating Current (AC) is a type of electrical current that varies sinusoidally with time.

- AC voltage:

$$V(t) = V_m \times \sin(\omega t)$$

Where,

V_m = peak voltage, ω = angular frequency

- A resistive load is an electrical component that resists the flow of current and converts electrical energy into heat.
- Common examples of resistive loads: incandescent bulbs, electric heaters, resistors.

Characteristics of Purely Resistive Load

- In a purely resistive circuit, the load contains only resistance (R); no inductance (L) or capacitance (C).
- The voltage and current are in the same phase.
- There is no phase difference ($\theta = 0^\circ$) between voltage and current.
- Power is completely dissipated as heat in the resistor.

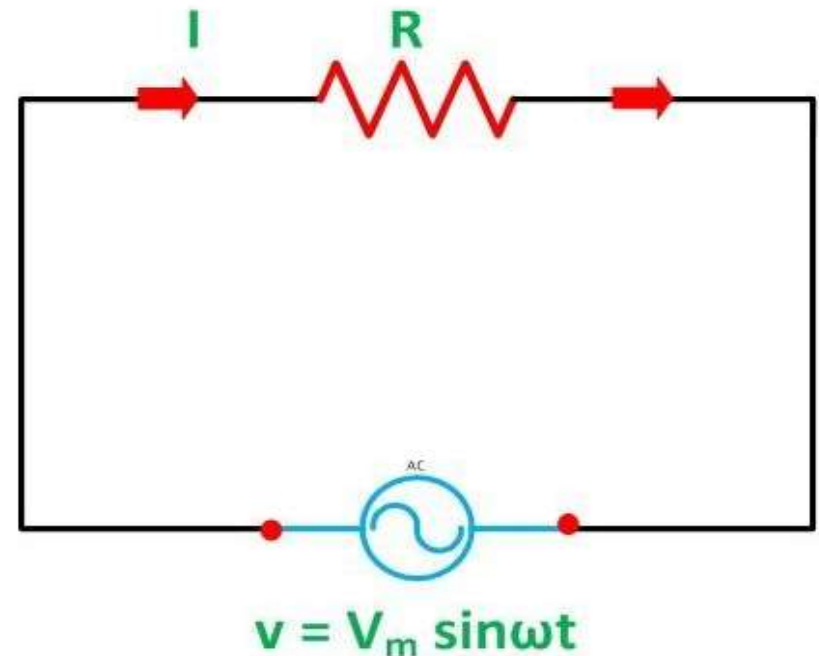


Figure 2.1 Purely Resistive Circuit

Voltage and Current Relationship

- Ohm's Law applies: $V = I \times R$

- If

$$V(t) = V_m \times \sin(\omega t),$$

Then Current:

$$i(t) = I_m \times \sin(\omega t)$$

where,

$$I_m = V_m / R$$

- Both voltage and current have identical waveforms and peak at the same time.
- No time lag or lead between voltage and current.

Phasor Representation

- Phasors are rotating vectors used to represent sinusoidal quantities.
- For a purely resistive load:
 - Voltage phasor (V) and current phasor (I) lie on the same axis.
- Phase angle $\theta = 0^\circ$
- No angular separation between phasors.

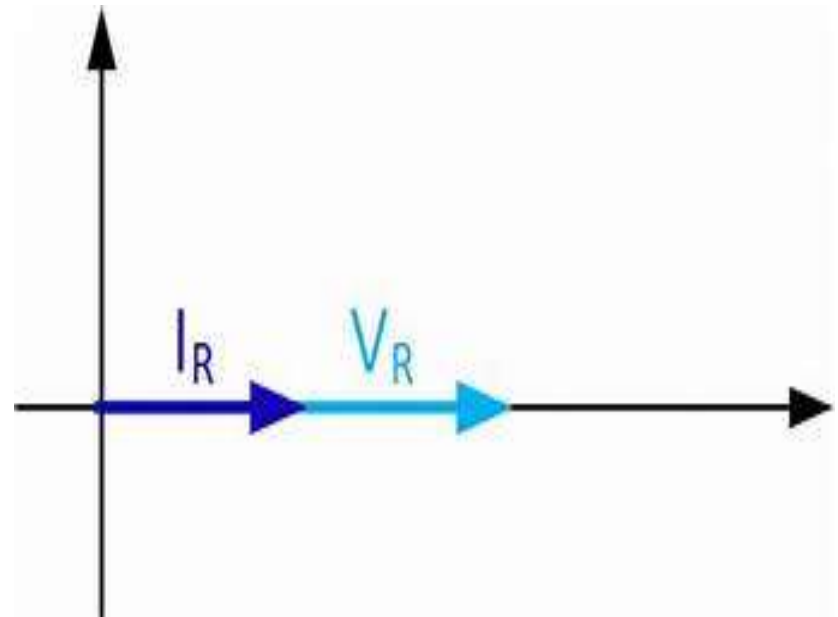


Figure 2.2 Phasor Diagram

Waveforms of Voltage and Current

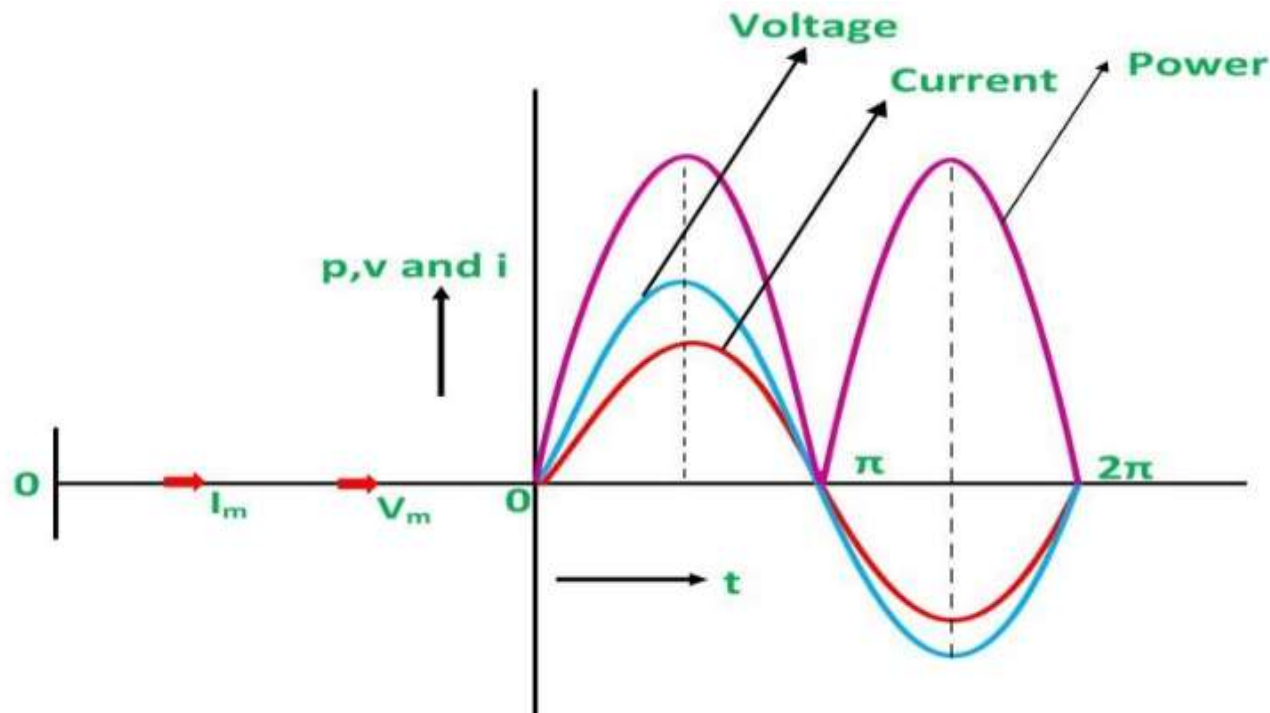


Figure 2.2 Waveform Diagram

- Both waveforms are sinusoidal and superimpose in time.
- Peak values of current and voltage occur simultaneously.

Power in Pure Resistive Load

- **Instantaneous Power:**

$$p(t) = v(t) \times i(t) = V_m \times I_m \times \sin^2(\omega t)$$

- Since $\sin^2(\omega t)$ is always positive, power is always positive.

- **Average Power (P)** over one cycle:

$$P = (V_m \times I_m) / 2 = V_{rms} \times I_{rms}$$

- Power is continuously consumed in the resistor and converted to heat.

Key Formulas:

$$V(t) = V_m \times \sin(\omega t)$$

$$I(t) = I_m \times \sin(\omega t)$$

$$P(t) = V_m \times I_m \times \sin^2(\omega t)$$

$$P_{avg} = (V_m \times I_m) / 2 = V_{rms} \times I_{rms}$$

Summary

- In a purely resistive AC circuit, voltage and current are in phase ($\theta = 0^\circ$).
- No reactive components \rightarrow no energy is stored or returned.
- Phasors of V and I align, indicating phase alignment.
- Power is always positive, indicating real power consumption.
- Useful for understanding basic power dissipation in AC resistive loads.

Parul[®]
University

NAAC
GRADE **A++**



<https://paruluniversity.ac.in/>



Analysis with phasor diagram of Purely Inductive Load

Meet Soni

Assistant Professor
Electrical Engineering

Content

1. Introduction to Inductance and AC Circuits	3
2. Characteristics of Purely Inductive Load	4
3. Voltage and Current Relationship	5
4. Phasor Representation	6
5. Waveforms of Voltage and Current	7
6. Power in Pure Inductive Load	8
7. Key Points / Summary	9

Introduction to Inductance and AC Circuits

- An inductor opposes changes in current and stores energy in a magnetic field.
- In AC circuits, the current continuously changes direction, and inductors exhibit inductive reactance (X_L).
- The inductive reactance is given by: $X_L = 2\pi fL$, where f = frequency, L = inductance in henry (H)
- A pure inductive load has only inductance, no resistance or capacitance.

Characteristics of Purely Inductive Load

- In a purely inductive circuit, current lags voltage by 90° ($\pi/2$ radians).
- The energy is alternately stored and released by the inductor; no real power is consumed.
- The circuit absorbs and returns power to the source each cycle.
- The average power consumed over a full cycle is zero.

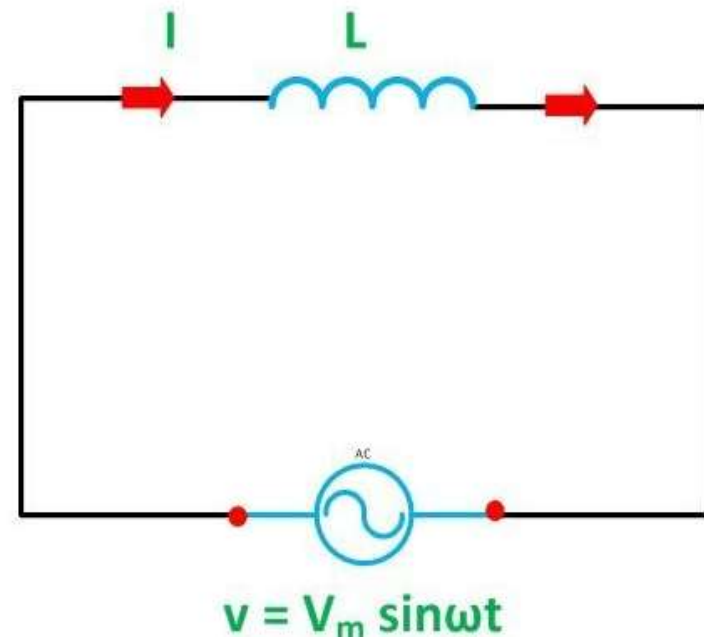


Figure 2.1 Purely Inductive Circuit

Voltage and Current Relationship

- Applied voltage:

$$v(t) = V_m \times \sin(\omega t)$$

- Current through pure inductor:

$$i(t) = I_m \times \sin(\omega t - 90^\circ) = I_m \times (-\cos(\omega t))$$

- Current lags the voltage by 90° due to inductive nature.
- Peak of current occurs **after** the peak of voltage.

Key Formula:

$$I_m = V_m / X_L,$$

where $X_L = 2\pi fL$

Phasor Representation

In phasor form:

- Voltage phasor **leads** the current phasor by 90°
- Alternatively, **current lags** the voltage phasor by 90°
- This 90° phase shift represents purely inductive behavior.

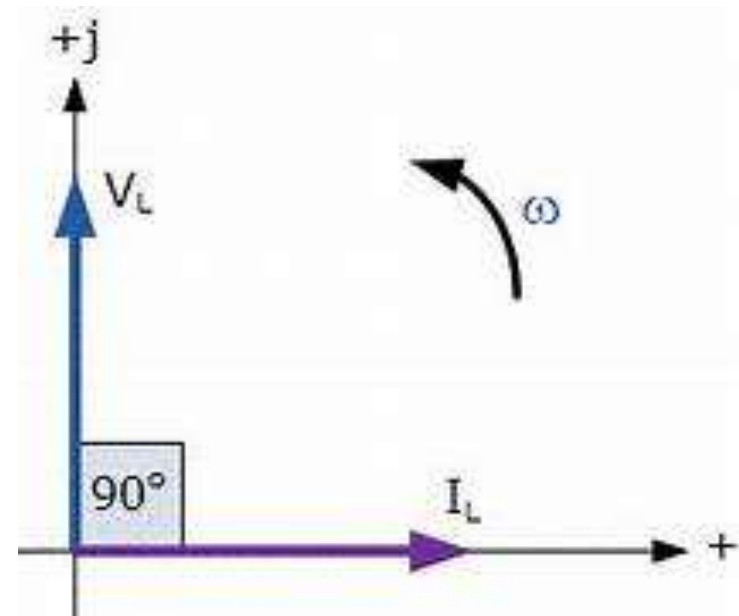


Figure 2.2 Phasor Diagram

Waveforms of Voltage and Current

- Voltage waveform: sinusoidal
- Current waveform: sinusoidal and lags voltage by 90°
- Zero crossing of current occurs after zero crossing of voltage.

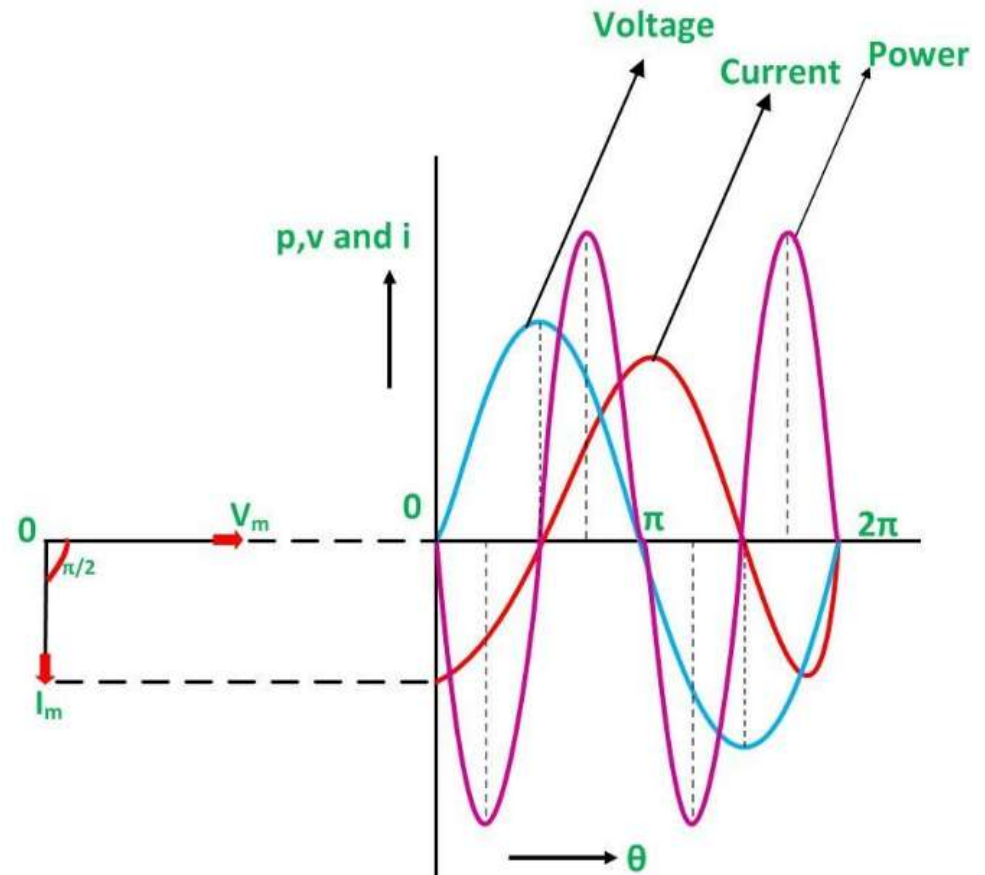


Figure 2.2 Waveform Diagram

Power in Pure Inductive Load

- **Instantaneous Power:**

$$p(t) = v(t) \times i(t) = V_m \times I_m \times \sin(\omega t) \times \sin(\omega t - 90^\circ)$$

$$p(t) = V_m \times I_m \times \sin(\omega t) \times (-\cos(\omega t))$$

$$p(t) = -V_m \times I_m \times \sin(\omega t) \times \cos(\omega t)$$

- This results in alternating positive and negative power.
- Average Power (P) = 0 (No net power consumed)

Important Observation:

- Power oscillates between source and inductor.
- Energy is stored and returned, not dissipated.

Summary

- In a purely inductive AC circuit, current lags voltage by 90° .
- Inductor stores energy in its magnetic field and returns it back.
- Phasor diagram shows 90° lag of current behind voltage.
- No real power is consumed; average power is zero.
- Circuit is reactive, and power oscillates within the system.

Parul[®]
University

NAAC
GRADE **A++**



<https://paruluniversity.ac.in/>



Analysis with phasor diagram of Purely Capacitive Load

Meet Soni

Assistant Professor
Electrical Engineering

Content

1. Introduction to Capacitance and AC Circuits	3
2. Characteristics of Purely Capacitive Load	4
3. Voltage and Current Relationship	5
4. Phasor Representation	6
5. Waveforms of Voltage and Current	7
6. Power in Pure Capacitive Load	8
7. Key Points / Summary	9

Introduction to Capacitance and AC Circuits

- A capacitor stores electrical energy in the form of an electric field between its plates.
- In an AC circuit, capacitors exhibit capacitive reactance (X_C) which opposes current flow.
- Capacitive reactance is given by: $X_C = 1 / (2\pi fC)$
where, f = frequency, C = capacitance in farads (F)
- A purely capacitive circuit contains only capacitance, with no resistance or inductance.

Characteristics of Purely Capacitive Load

- In a purely capacitive AC circuit, current leads voltage by 90° ($\pi/2$ radians).
- The capacitor charges and discharges every half-cycle.
- No real power is consumed; energy is stored and then returned.
- The average power over a full cycle is zero.

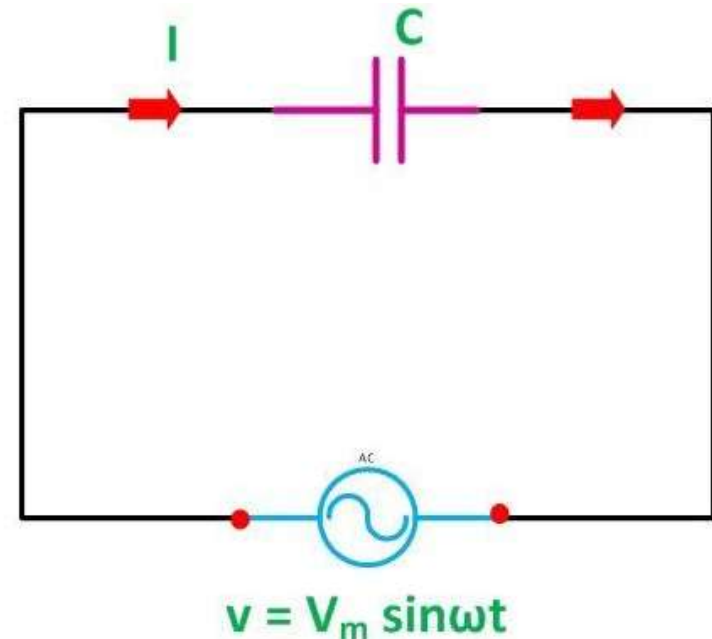


Figure 2.1 Purely Capacitive Circuit

Voltage and Current Relationship

- Applied voltage:

$$v(t) = V_m \times \sin(\omega t)$$

- Current through pure capacitor:

$$i(t) = I_m \times \sin(\omega t + 90^\circ) = I_m \times \cos(\omega t)$$

- Current leads voltage by 90° in time domain.
- Peak current occurs before the peak voltage.

Key Formula:

$$I_m = V_m / X_C, \text{ where } X_C = 1 / (2\pi fC)$$

Phasor Representation

In phasor form:

- Current phasor leads voltage phasor by 90°
- This lead represents capacitive nature of the load
- Voltage lags behind current in purely capacitive circuit

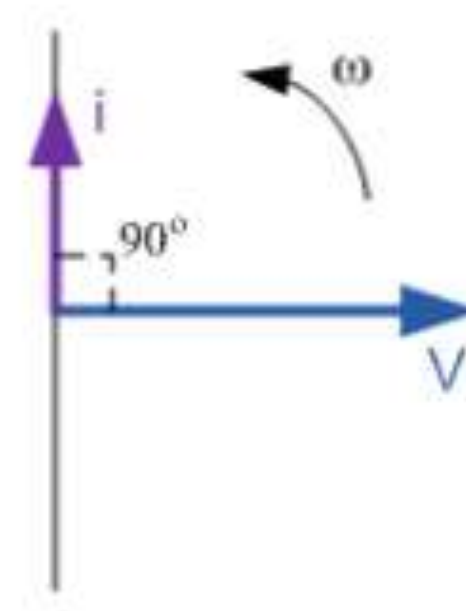


Figure 2.2 Phasor Diagram

Waveforms of Voltage and Current

- Voltage waveform is sinusoidal.
- Current waveform is sinusoidal and leads the voltage by 90° .
- Zero crossing of current occurs before that of voltage.

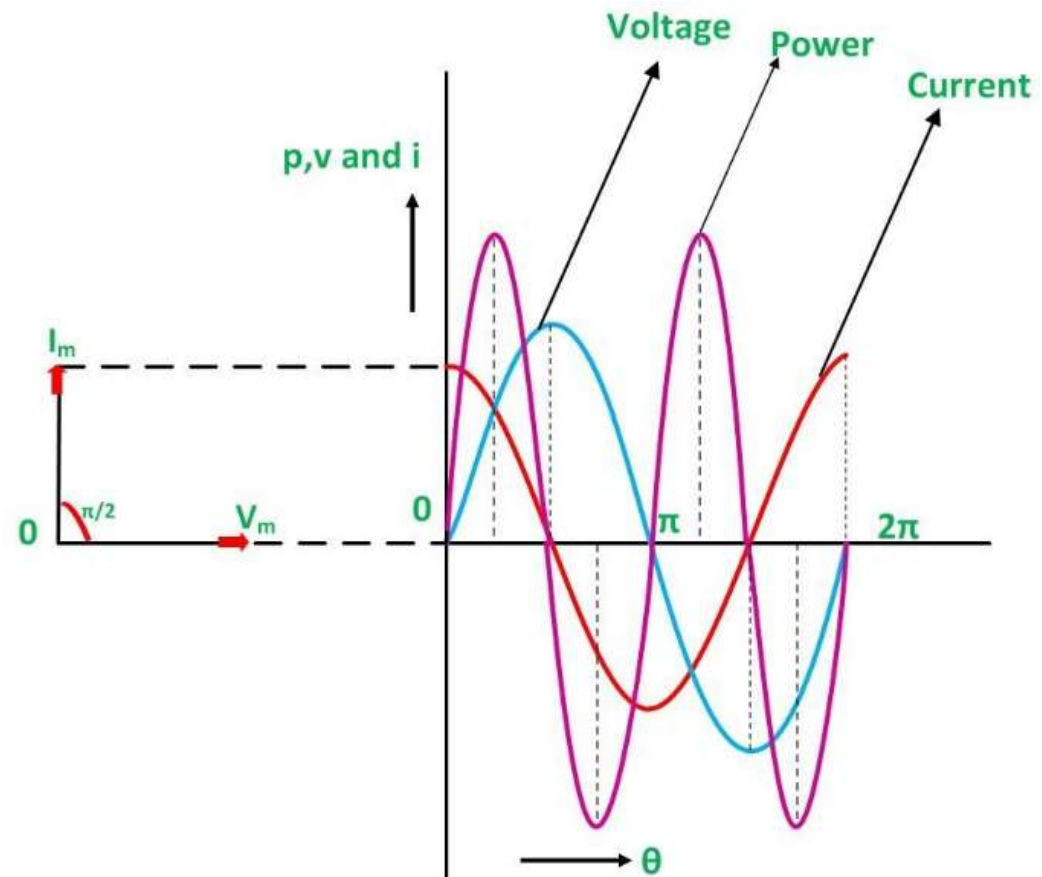


Figure 2.2 Waveform Diagram

Power in Pure Capacitive Load

- **Instantaneous Power:**

$$p(t) = v(t) \times i(t) = V_m \times I_m \times \sin(\omega t) \times \sin(\omega t + 90^\circ)$$

$$p(t) = V_m \times I_m \times \sin(\omega t) \times \cos(\omega t)$$

$$p(t) = V_m \times I_m \times 0.5 \times \sin(2\omega t)$$

- Power alternates between positive and negative values.
- Average Power (P) = 0 over one full cycle.

Key Insight:

- Energy is not dissipated but is stored and returned to the source cyclically.

Summary

- In a purely capacitive circuit, current leads voltage by 90° .
- The capacitor stores and returns energy every cycle.
- Phasor diagram shows current ahead of voltage.
- No real power is consumed; only reactive power is present.
- Capacitors offer capacitive reactance (X_C) which decreases with frequency.

Parul[®]
University

NAAC
GRADE **A++**



<https://paruluniversity.ac.in/>



Analysis with phasor diagram of RL Series Load

Meet Soni

Assistant Professor
Electrical Engineering

Content

1. Introduction to RL Series Circuit	3
2. Impedance in RL Circuit	4
3. Voltage and Current Relationship	5
4. Phasor Representation	6
5. Waveforms of Voltage and Current	7
6. Power in RL Circuit	8
7. Power Factor and Phase Angle	9
8. Key Points / Summary	10

Introduction to RL Series Circuit

- An RL series circuit contains a resistor (R) and an inductor (L) connected in series.
- When supplied with an AC source, both elements influence the total behavior:
 1. Resistor causes voltage drop in phase with current.
 2. Inductor causes voltage drop leading the current by 90° .
- The total current is common through both R and L.

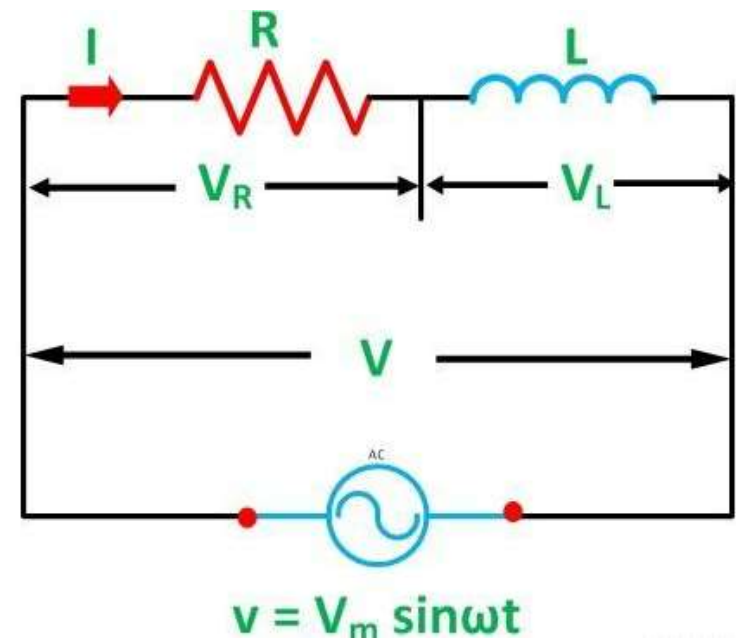


Figure 2.1 RL Series Circuit

Impedance in RL Circuit

- The total opposition offered to AC is called impedance (Z).
- Impedance in an RL circuit is given by:

$$Z = \sqrt{R^2 + XL^2}$$

Where, $XL = 2\pi fL$

- The circuit behaves partly resistive and partly inductive.

Key Formula:

$$I = V / Z,$$

- Where,
V = applied voltage,
Z = total impedance

Voltage and Current Relationship

- Current in the RL circuit lags the applied voltage by a phase angle ϕ .
- The phase angle is determined by the relative values of R and XL.

$$\tan(\phi) = X_L / R$$

Current Equation:

$$i(t) = I_m \times \sin(\omega t - \phi)$$

$$I_m = V_m / Z$$

Phasor Representation

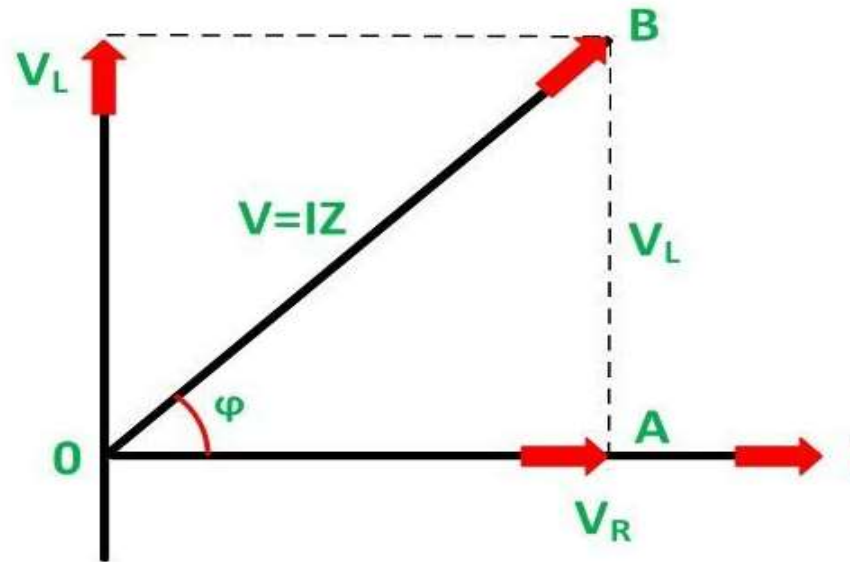


Figure 2.2 Phasor Diagram

- The voltage drop across R (V_R) is in phase with the current.
- The voltage drop across L (V_L) leads the current by 90° .
- The total applied voltage (V) is the phasor sum of V_R and V_L .

Waveforms of Voltage and Current

- The current waveform lags behind the voltage waveform by angle ϕ .
- Waveforms are sinusoidal but not in phase.
- The degree of lag depends on the R to L ratio.

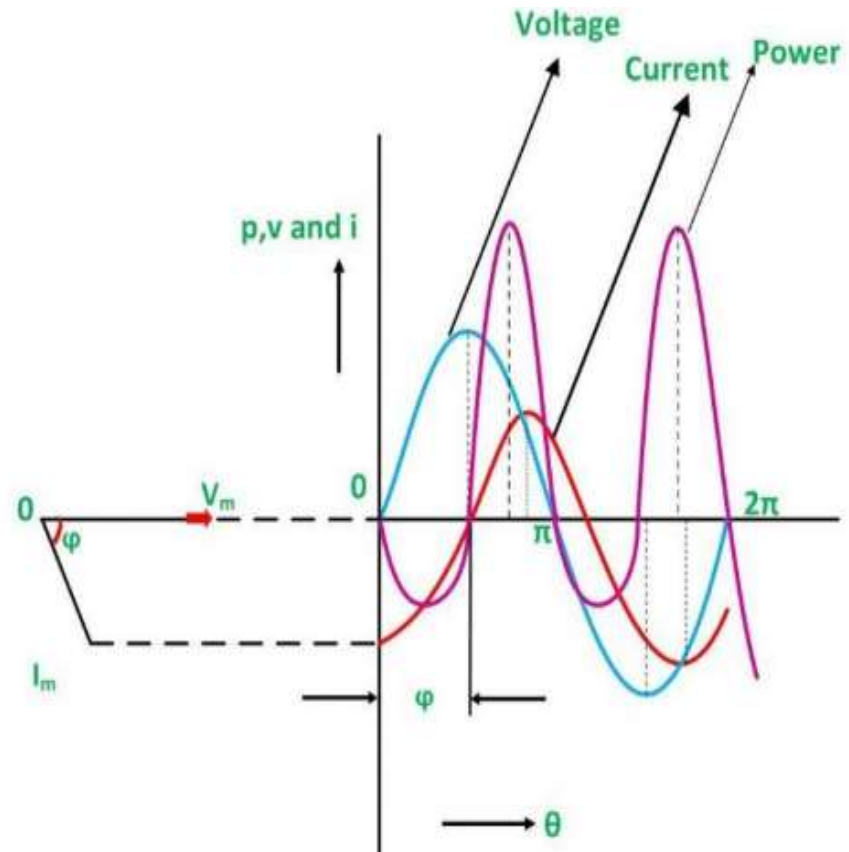


Figure 2.2 Waveform Diagram

Power in RL Circuit

- **Instantaneous Power:**

$$p(t) = v(t) \times i(t)$$

- **True (Active) Power:**

$$P = VI \times \cos(\varphi) \text{ (Measured in watts)}$$

- **Reactive Power (Q):**

$$Q = VI \times \sin(\varphi) \text{ (Measured in VAR)}$$

- **Apparent Power (S):**

$$S = VI \text{ (Measured in VA)}$$

Note:

- Only the resistive part consumes real power.
- Inductive part causes reactive power flow.

Power Factor and Phase Angle

- Power Factor (PF) = $\cos(\phi)$

It indicates the efficiency of power usage.

- ϕ is the phase angle between applied voltage and current.
- If X_L increases (i.e., more inductive), PF decreases.

Good to Know:

- A low PF implies high reactive power, causing inefficiency.
- Ideal PF = 1 (purely resistive)

Summary

- RL series circuit contains both resistance and inductance.
- Impedance (Z) is the vector sum of R and X_L .
- Current lags voltage by an angle ϕ .
- Power factor depends on R to X_L ratio.
- Only resistive element consumes real power.
- Phasor diagram and waveforms help in visualizing the phase relationship.

Parul[®]
University

NAAC
GRADE **A++**



<https://paruluniversity.ac.in/>



Analysis with phasor diagram of RC Series Load

Meet Soni

Assistant Professor
Electrical Engineering

Content

1. Introduction to RC Series Circuit	3
2. Impedance in RC Circuit	4
3. Voltage and Current Relationship	5
4. Phasor Representation	6
5. Waveforms of Voltage and Current	7
6. Power in RC Circuit	8
7. Power Factor and Phase Angle	9
8. Key Points / Summary	10

Introduction to RC Series Circuit

- An RC series circuit contains a resistor (R) and a capacitor (C) connected in series.
- When connected to an AC source:
 1. Resistor causes voltage drop in phase with current.
 2. Capacitor causes voltage drop that lags the current by 90° .
- The total current flows through both R and C.

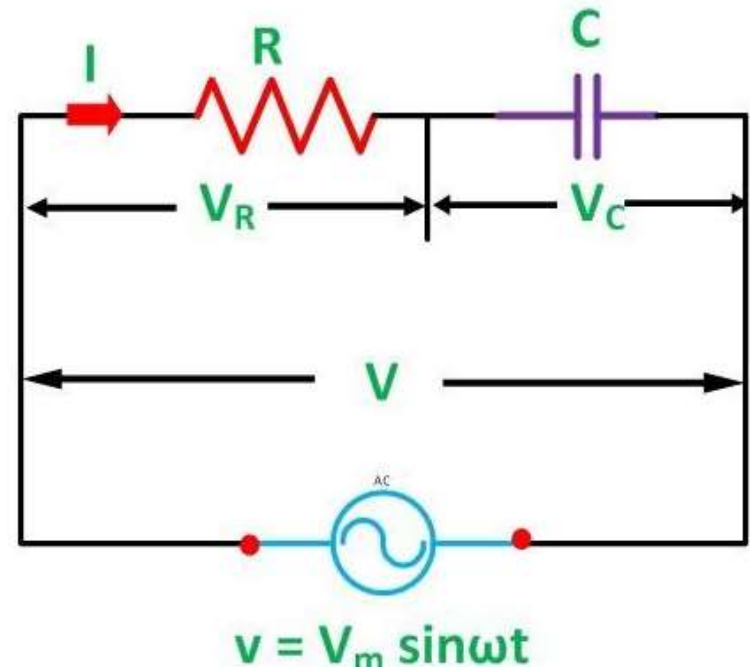


Figure 2.1 RC Series Circuit

Impedance in RC Circuit

- The total opposition in an RC circuit is the impedance (Z).

- Impedance is calculated using:

$$Z = \sqrt{R^2 + X_C^2}$$

Where, $X_C = 1 / (2\pi fC)$

- Capacitive reactance decreases with increasing frequency.

Key Formula:

$$I = V / Z$$

Voltage and Current Relationship

- The current leads the applied voltage by a phase angle ϕ .
- The phase angle depends on the relative values of R and XC.

$$\tan(\phi) = -XC / R$$

Current Equation:

$$I(t) = I_m \times \sin(\omega t + \phi)$$

$$I_m = V_m / Z$$

Phasor Representation

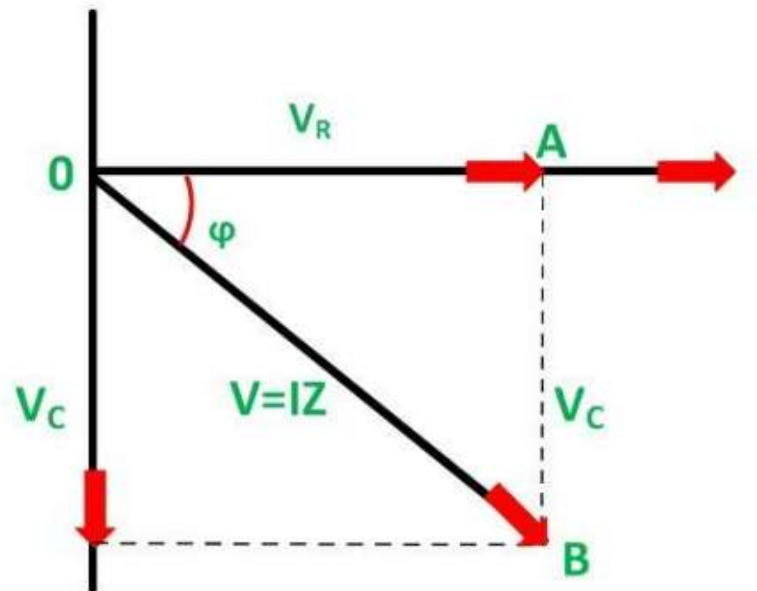


Figure 2.2 Phasor Diagram

- Voltage across resistor (V_R) is in phase with current.
- Voltage across capacitor (V_C) lags the current by 90° .
- Total voltage is the phasor sum of V_R and V_C .

Waveforms of Voltage and Current

- Voltage and current are sinusoidal but not in phase.
- Current leads voltage by phase angle ϕ .
- The lead depends on the ratio of R and XC.

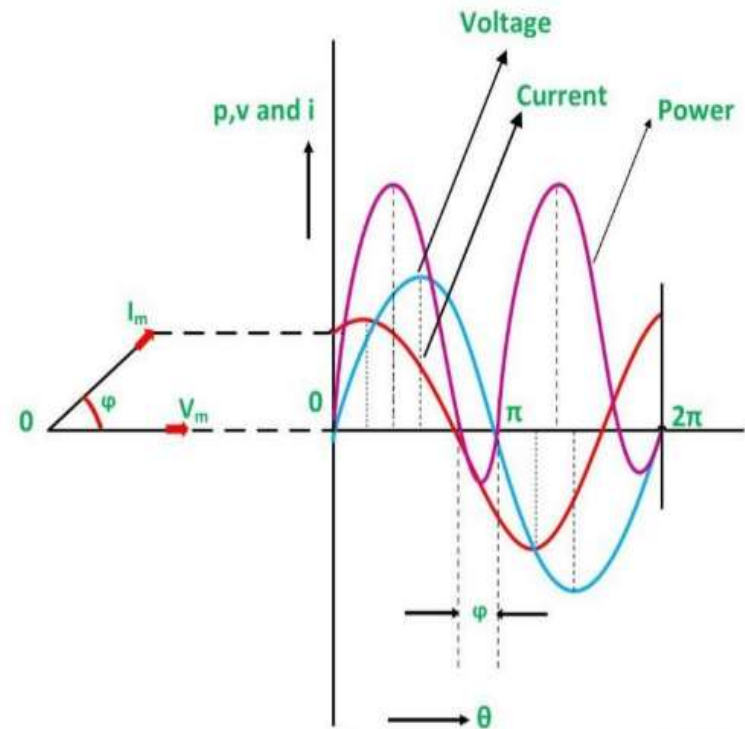


Figure 2.2 Waveform Diagram

Power in RC Circuit

- **Instantaneous Power:**

$$p(t) = v(t) \times i(t)$$

- **True (Active) Power:**

$$P = VI \times \cos(\varphi) \text{ (Measured in watts)}$$

- **Reactive Power (Q):**

$$Q = VI \times \sin(\varphi) \text{ (Measured in VAR)}$$

- **Apparent Power (S):**

$$S = VI \text{ (Measured in VA)}$$

Note:

- Only the resistive part consumes real power.
- Capacitor only causes energy storage and return.

Power Factor and Phase Angle

- Power Factor (PF) = $\cos(\phi)$

Measures the efficiency of power usage.

- In an RC circuit, ϕ is negative, indicating leading current.
- High $X_C \rightarrow$ High phase angle \rightarrow Low PF

Important:

- A high-power factor means better energy efficiency.

Summary

- RC series circuit consists of a resistor and a capacitor in series.
- Impedance is calculated using vector addition of R and XC.
- Current leads voltage by angle ϕ .
- Only resistor consumes real power; capacitor causes reactive power.
- Power factor depends on R and XC.
- Phasor diagrams and waveforms clarify phase relationships.

Parul[®]
University

NAAC
GRADE **A++**



<https://paruluniversity.ac.in/>



Analysis with phasor diagram of RLC Series Load

Meet Soni

Assistant Professor
Electrical Engineering

Content

1. Introduction to RLC Series Circuit	3
2. Impedance in RLC Circuit	4
3. Voltage and Current Relationship	5
4. Phasor Representation	6
5. Waveforms of Voltage and Current	7
6. Power in RLC Circuit	8
7. Resonance in RLC Circuit	9
8. Power Factor and Phase Angle	10
9. Key Points / Summary	11

Introduction to RLC Series Circuit

- An RLC series circuit contains a resistor (R), inductor (L), and capacitor (C) connected in series.
- It combines the effects of resistance, inductance, and capacitance.
- The behavior of the circuit depends on the relative values of L and C.

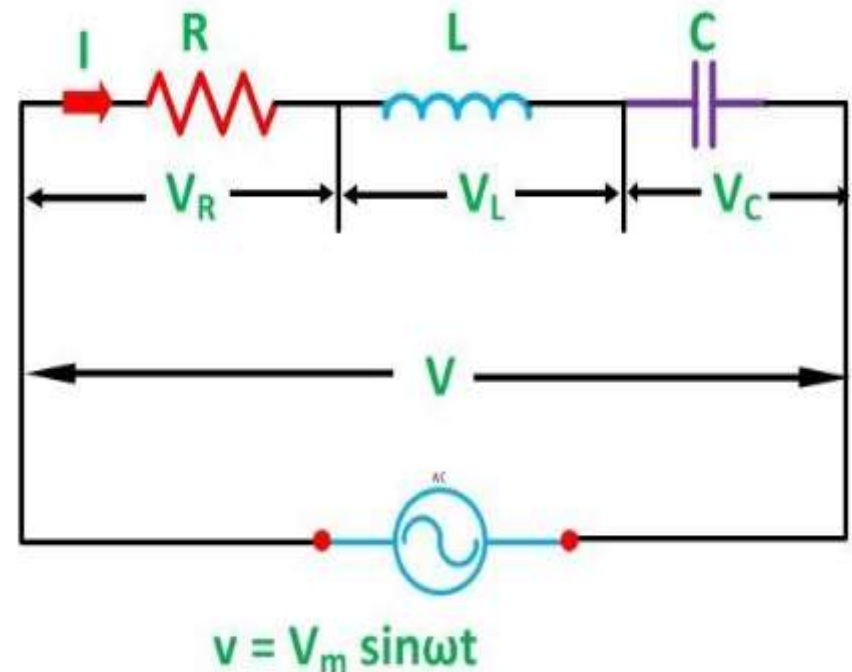


Figure 2.1 RLC Series Circuit

Impedance in RLC Circuit

- Total impedance (Z) is given by:

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

where:

$$X_L = 2\pi fL \text{ and } X_C = 1 / (2\pi fC)$$

- Net reactance ($X = X_L - X_C$) can be:
 - Positive \rightarrow Inductive circuit
 - Negative \rightarrow Capacitive circuit
 - Zero \rightarrow Resonant circuit

Current Magnitude:

$$I = V / Z$$

Voltage and Current Relationship

- Depending on net reactance, current either lags, leads, or is in phase with voltage.

$$\tan(\varphi) = (X_L - X_C) / R$$

Current Equation:

$$i(t) = I_m \times \sin(\omega t \pm \varphi)$$

(Sign depends on inductive or capacitive nature)

Phasor Representation

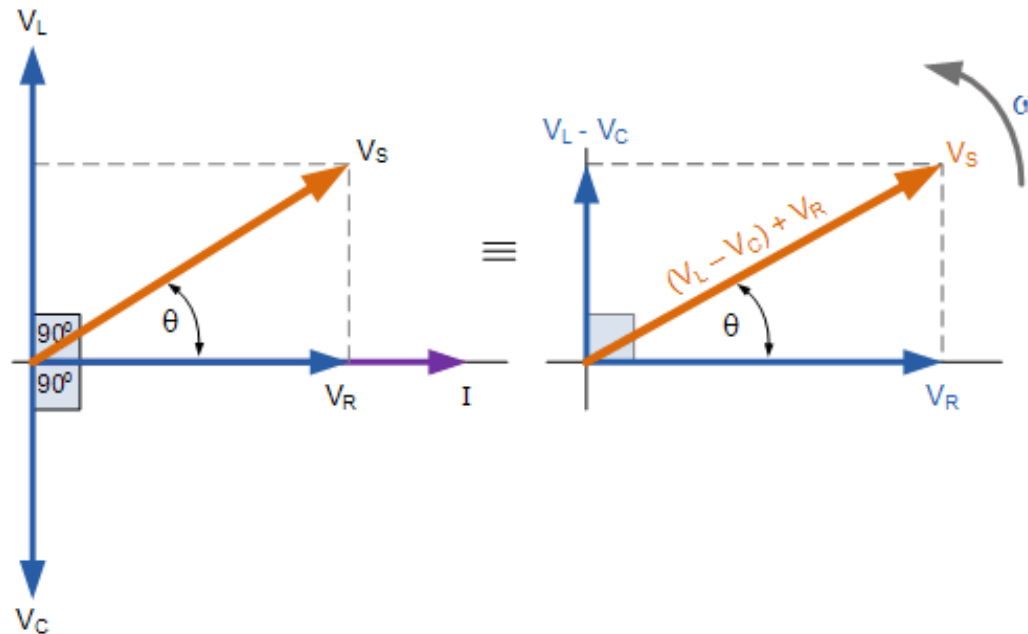


Figure 2.2 Phasor Diagram

- V_R is in phase with current.
- V_L leads the current by 90° .
- V_C lags the current by 90° .
- Net reactive voltage = $V_L - V_C$

Waveforms of Voltage and Current

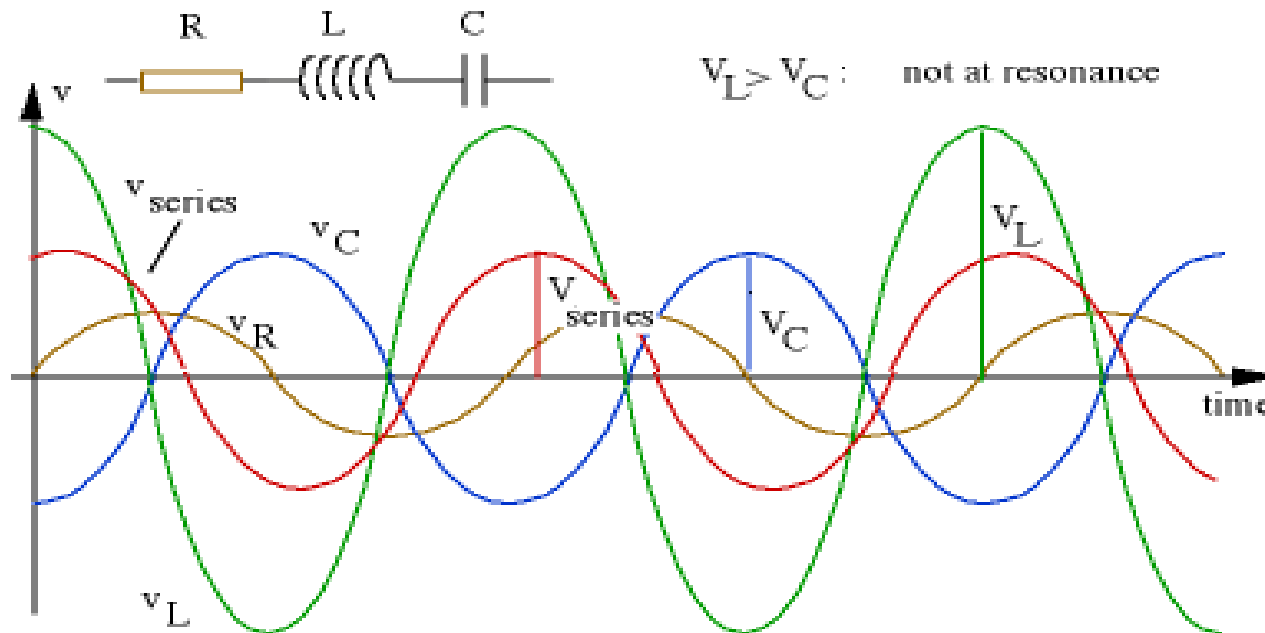


Figure 2.2 Waveform Diagram

- Current waveform varies in phase with applied voltage depending on net reactance.
- At resonance, current is in phase with voltage (purely resistive behavior).

Power in RLC Series Circuit

- **Instantaneous Power:**

$$p(t) = v(t) \times i(t)$$

- **True (Active) Power:**

$$P = VI \times \cos(\varphi) \text{ (Measured in watts)}$$

- **Reactive Power (Q):**

$$Q = VI \times \sin(\varphi) \text{ (Measured in VAR)}$$

- **Apparent Power (S):**

$$S = VI \text{ (Measured in VA)}$$

Note:

- Power is dissipated only by the resistor.
- Inductor and capacitor store and release energy without dissipation.

Resonance in RLC Circuit

- Resonance occurs when $X_L = X_C$, making net reactance zero.

- At resonance:

- $Z = R$ (minimum)
- Current is maximum
- Power factor = 1

- Resonant Frequency (f_r):

$$f_r = 1 / (2\pi\sqrt{LC})$$

Important:

- Resonance improves circuit efficiency and is useful in tuning applications.

Power Factor and Phase Angle

- Power Factor (PF) = $\cos(\phi)$
- ϕ depends on $(X_L - X_C) / R$
- PF = 1 at resonance
- Inductive circuit \rightarrow PF lagging
- Capacitive circuit \rightarrow PF leading

Key Insight:

- Better power factor means better energy utilization and reduced losses.

Summary

- RLC circuit combines R, L, and C in series.
- Total impedance depends on R and net reactance ($X_L - X_C$).
- Current can lead, lag, or be in phase with voltage.
- Resonance occurs when $X_L = X_C$, resulting in maximum current and unity power factor.
- Real power is consumed only by R; L and C exchange reactive power.
- Applications include filters, oscillators, and tuning circuits.

Parul[®]
University

NAAC
GRADE **A++**



<https://paruluniversity.ac.in/>



Analysis with phasor diagram of RL Parallel Load

Meet Soni

Assistant Professor
Electrical Engineering

Content

1. Introduction to RL Parallel Circuit	3
2. Behavior of RL Branches in Parallel	4
3. Current Distribution and Impedance	5
4. Phasor Representation	6
5. Waveforms of Current and Voltage	7
6. Power in RL Parallel Circuit	8
7. Power Factor and Phase Angle	9
8. Key Points / Summary	10

Introduction to RL Parallel Circuit

- An RL parallel circuit has a resistor (R) and inductor (L) connected in parallel across an AC voltage source.
- The voltage across both branches is the same.
- The total current is the phasor sum of current through R and current through L.

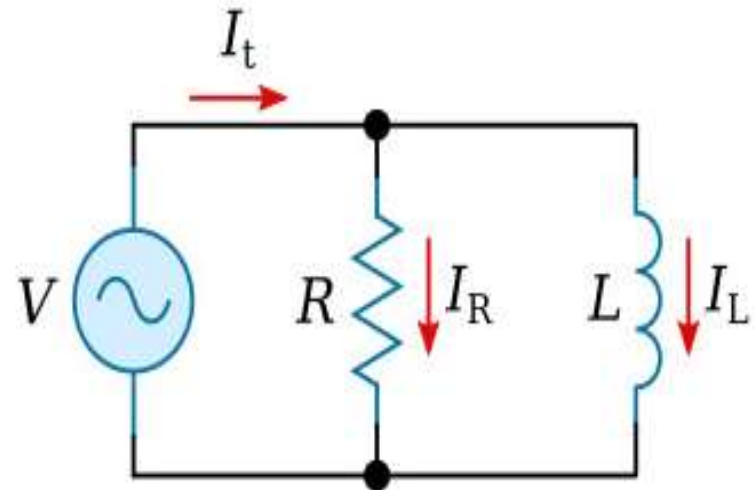


Figure 2.1 RL parallel Circuit

Behavior of RL Branches in Parallel

- Resistive branch current (I_R) is in phase with voltage.
- Inductive branch current (I_L) lags behind voltage by 90° .
- The resulting current is neither in phase nor 90° lagging, but has a phase angle ϕ .

Current Distribution and Impedance

- Total current (I_T) is calculated using phasor addition:

$$I_T = \sqrt{I_R^2 + I_L^2}$$

- Branch currents:

$$I_R = V / R$$

$$I_L = V / X_L, \text{ where } X_L = 2\pi fL$$

- The total impedance (Z) is not just a scalar sum.

Admittance (Y) is used for easier analysis:

$$Y = \sqrt{G^2 + B^2},$$

Where,

$G = 1 / R$ (conductance),

$B = 1 / X_L$ (susceptive part)

Phasor Representation

- Voltage (V) is taken as reference (horizontal axis).
- I_R is in phase with V (horizontal phasor).
- I_L lags behind V by 90° (vertical downward phasor).
- I_T is the phasor sum of I_R and I_L .

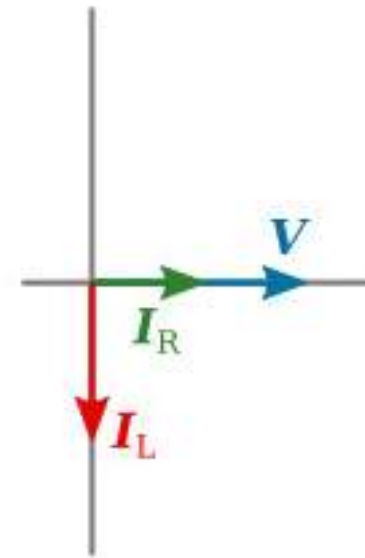


Figure 2.2 Phasor Diagram

Waveforms of Voltage and Current

- Voltage remains common and sinusoidal across both branches.
- i_R follows voltage waveform.
- i_L lags voltage waveform by 90° .

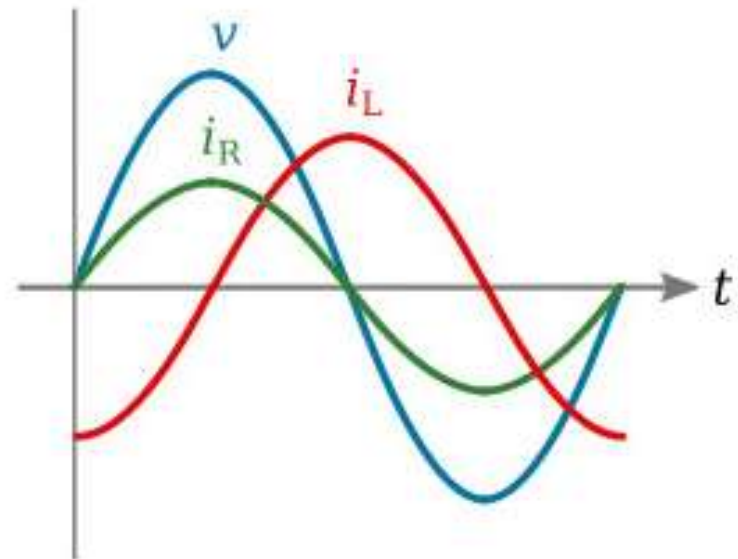


Figure 2.2 Waveform Diagram

Power in RL Parallel Circuit

- **Instantaneous Power:**

$$p(t) = v(t) \times i(t)$$

- **Real Power (P)** is consumed only in resistive branch:

$$P = V \times IR = V^2 / R$$

- **Reactive Power (Q)** is associated with the inductor:

$$Q = V \times IL = V^2 / XL$$

- **Apparent Power (S):**

$$S = V \times IT$$

Power Factor and Phase Angle

- Power Factor (PF) = $\cos(\phi)$, where ϕ is the angle between total current and voltage.
- ϕ is positive (lagging) due to inductive effect.
- Higher XL \rightarrow higher phase lag \rightarrow lower PF
- Improving PF can reduce losses and increase efficiency.

Summary

- RL parallel circuit shares common voltage, but branch currents differ in phase.
- IR is in phase with V; IL lags behind by 90° .
- Total current is phasor sum of IR and IL.
- Only resistor consumes real power.
- Power factor is lagging due to inductance.
- Useful in analyzing filter circuits, tuning applications, and AC analysis.

Parul[®]
University

NAAC
GRADE **A++**



<https://paruluniversity.ac.in/>



Analysis with phasor diagram of RC Parallel Load

Meet Soni

Assistant Professor
Electrical Engineering

Content

1. Introduction to RC Parallel Circuit 3
2. Behavior of RC Branches in Parallel 4
3. Current Distribution and Impedance 5
4. Phasor Representation 6
5. Waveforms of Current and Voltage 7
6. Power in RC Parallel Circuit 8
7. Power Factor and Phase Angle 9
8. Key Points / Summary 10

Introduction to RC Parallel Circuit

- An RC parallel circuit has a resistor (R) and capacitor (C) connected in parallel across an AC supply.
- The voltage is common to both branches.
- The total current is the phasor sum of currents in R and C branches.

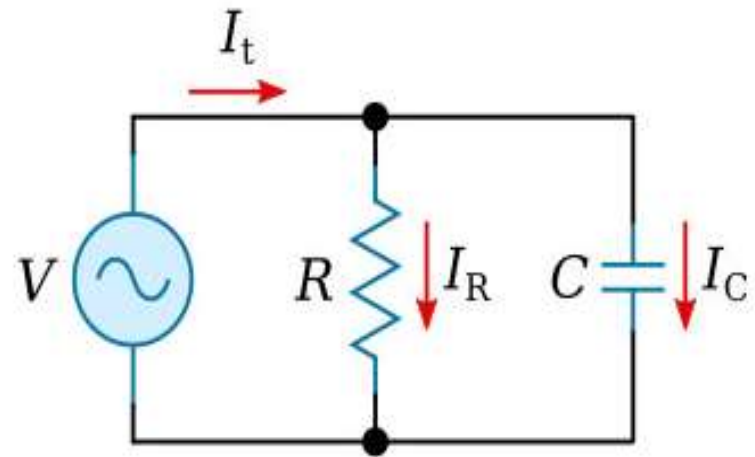


Figure 2.1 RC parallel Circuit

Behavior of RC Branches in Parallel

- I_R (Resistor current) is in phase with the voltage.
- I_C (Capacitor current) leads the voltage by 90° .
- The resultant current leads the voltage by an angle ϕ depending on relative magnitudes of I_R and I_C .

Current Distribution and Impedance

- Branch currents:

$$I_R = V / R$$

$$I_C = V / X_C, \text{ where } X_C = 1 / (2\pi fC)$$

- Total current (I_T) is the phasor sum:

$$I_T = \sqrt{I_R^2 + I_C^2}$$

Admittance (Y):

$$Y = \sqrt{G^2 + B^2}$$

where:

$G = 1 / R$ (conductance),

$B = 2\pi fC$ (capacitive susceptance)

Phasor Representation

- Voltage is the reference phasor (horizontal).
- I_R is in phase with V (horizontal).
- I_C leads V by 90° (vertical upward).
- I_T is the phasor resultant of I_R and I_C .

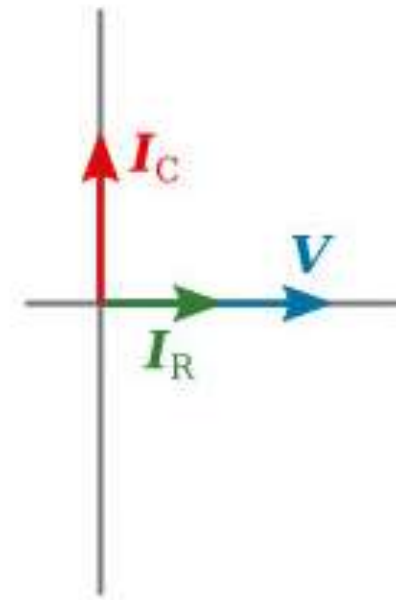


Figure 2.2 Phasor Diagram

Waveforms of Voltage and Current

- Voltage across both branches remains sinusoidal and common.
- I_R is in phase with voltage.
- I_C leads voltage by 90° .

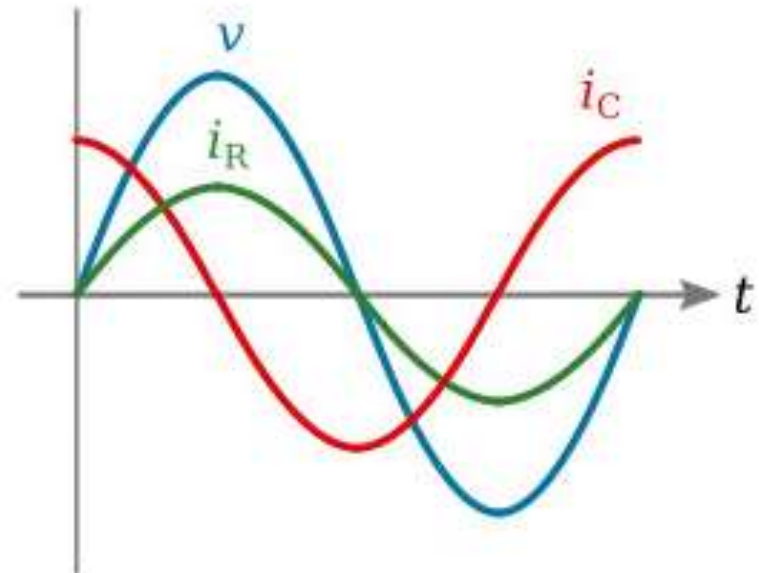


Figure 2.2 Waveform Diagram

Power in RL Parallel Circuit

- **Instantaneous Power:**

$$p(t) = v(t) \times i(t)$$

- **Real Power (P)** is consumed only in resistive branch:

$$P = V \times IR = V^2 / R$$

- **Reactive Power (Q)** is associated with the inductor:

$$Q = V \times IC = V^2 / XC$$

- **Apparent Power (S):**

$$S = V \times IT$$

Power Factor and Phase Angle

- Power Factor (PF) = $\cos(\phi)$
- ϕ is the phase angle between total current and voltage.
- PF is leading due to capacitive current.
- High capacitance or frequency \rightarrow higher IC \rightarrow greater lead \rightarrow lower PF

Summary

- RC parallel circuit consists of R and C in parallel across an AC source.
- Voltage remains common, but currents differ in phase.
- I_R is in phase; I_C leads by 90° .
- Total current leads voltage \rightarrow leading power factor.
- Power is dissipated only in resistor, not in capacitor.
- Widely used in filtering, signal shaping, and tuning.

Parul[®]
University

NAAC
GRADE **A++**



<https://paruluniversity.ac.in/>



Analysis with phasor diagram of RLC Parallel Load

Meet Soni

Assistant Professor
Electrical Engineering

Content

1. Introduction to RLC Parallel Circuit 3
2. Nature of Components and Current Flow 4
3. Branch Currents and Admittance 5
4. Phasor Representation 6
5. Resonance in RLC Parallel Circuit 7
6. Voltage and Current Waveforms 8
7. Power and Power Factor 9
8. Key Points / Summary 10

Introduction to RLC Parallel Circuit

- An RLC parallel circuit has a resistor (R), inductor (L), and capacitor (C) connected in parallel across an AC voltage source.
- All components share the same voltage.
- The total current is the phasor sum of I_R , I_L , and I_C .

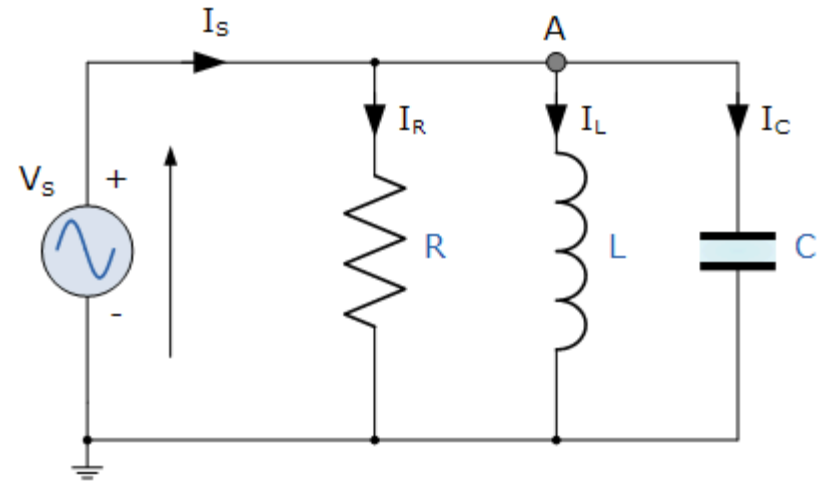


Figure 2.1 RLC parallel Circuit

Nature of Components and Current Flow

- I_R is in phase with voltage.
- I_L lags voltage by 90° .
- I_C leads voltage by 90° .
- Net reactive current: $I_X = I_C - I_L$
- Total current $I_T = I_R + I_X$ (phasor sum)

Branch Currents and Admittance

- Individual branch currents:

$$I_R = V / R$$

$$I_L = V / X_L, \text{ where } X_L = 2\pi fL$$

$$I_C = V / X_C, \text{ where } X_C = 1 / (2\pi fC)$$

- Use Admittance (Y) for calculation:

$$Y = \sqrt{G^2 + (BC - BL)^2}$$

where:

$$G = 1 / R$$

$$BC = 2\pi fC,$$

$$BL = 1 / (2\pi fL)$$

Phasor Representation

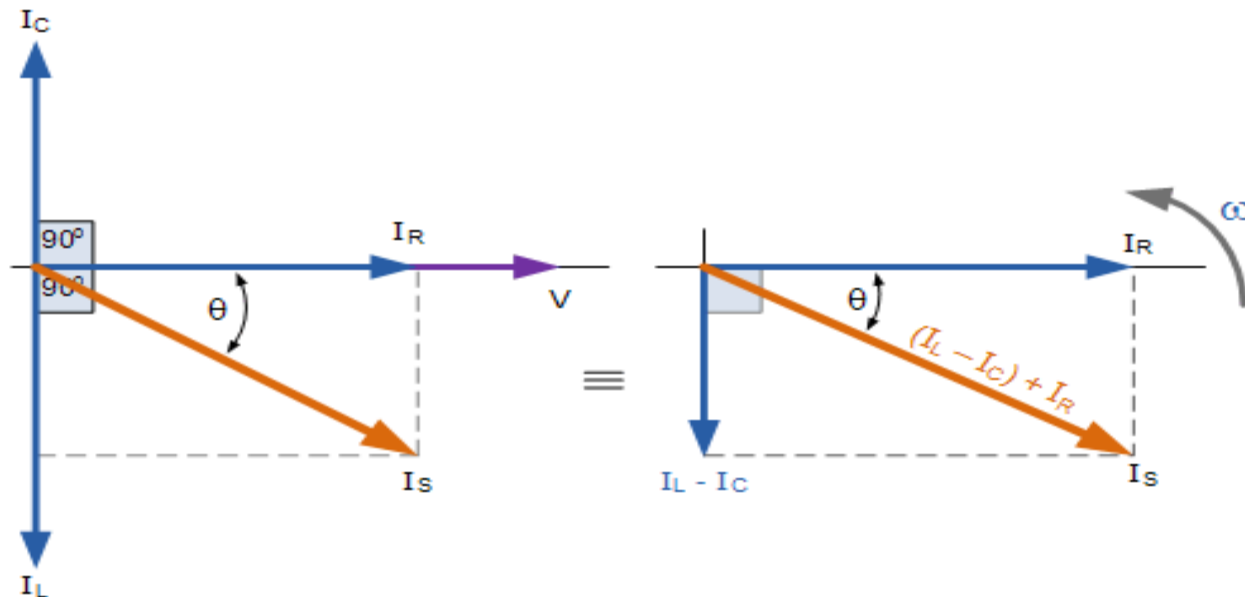


Figure 2.2 Phasor Diagram

- V is taken as reference phasor.
- I_R is in phase with V (horizontal).
- I_L lags V by 90° (downward).
- I_C leads V by 90° (upward).
- Net reactive current = $I_C - I_L$
- I_T is resultant phasor of I_R and I_X .

Resonance in RLC Parallel Circuit

- Resonance occurs when inductive reactance = capacitive reactance
i.e., $X_L = X_C$

- At resonance:

$$I_C = I_L \rightarrow I_X = 0, \text{ so } I_T = I_R$$

- Power factor becomes unity (purely resistive).
- Minimum line current at resonance.

Voltage and Current Waveforms

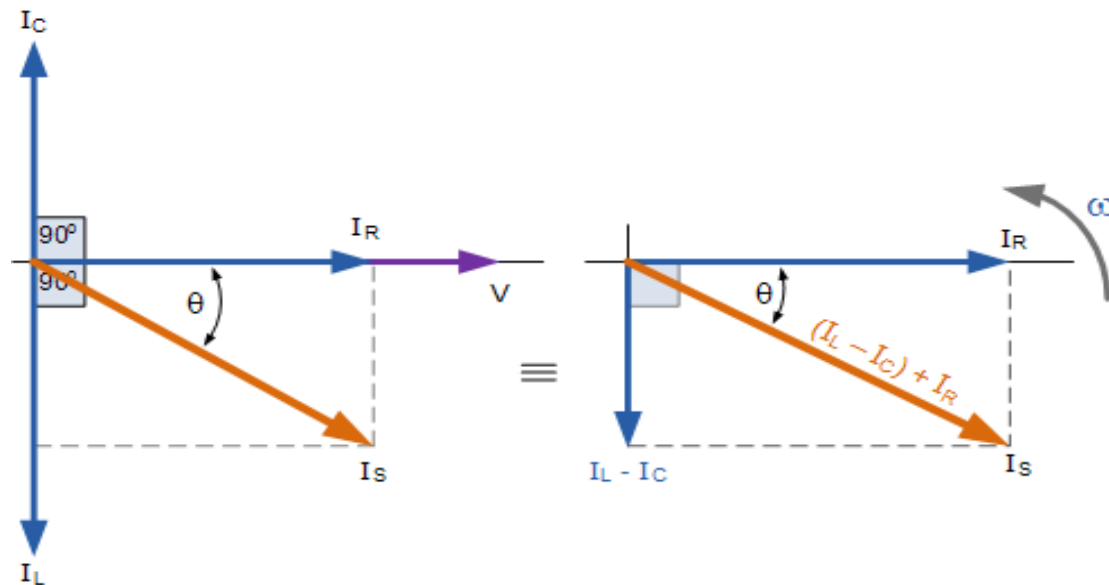


Figure 2.3 Waveform Diagram

- Voltage remains sinusoidal and same across all elements.
- I_R follows $V(t)$, I_L lags $V(t)$ by 90° , I_C leads $V(t)$ by 90° .

Power and Power Factor

- **Real Power (P):**

$$P = V^2 / R$$

- **Reactive Power (Q):**

$$Q = V^2 \times (1 / X_L - 1 / X_C)$$

- **Apparent Power (S):**

$$S = V \times IT$$

- **Power Factor (PF):**

$$PF = \cos(\varphi)$$

- Leading, lagging, or unity based on net reactance.

Summary

- RLC parallel circuit has R, L, and C in parallel with AC source.
- All components share common voltage, but branch currents differ in phase.
- Total current is phasor sum of I_R , I_L , and I_C .
- Resonance occurs when $X_L = X_C$, and current is minimized.
- Power factor depends on whether circuit is capacitive, inductive, or resistive.
- Useful in parallel resonance applications, filters, and tuned circuits.

Parul[®]
University

NAAC
GRADE **A++**



<https://paruluniversity.ac.in/>



Concept of Impedance, Admittance, Conductance, and Susceptance

Meet Soni

Assistant Professor
Electrical Engineering

Content

1.Introduction	3
2.Impedance (Z)	4
3.Admittance (Y)	5
4.Conductance (G)	6
5.Susceptance (B)	7
6.Mathematical Relationships	8
7.Phase Domain View	9
8.Key Points / Summary	10

Introduction

- These four terms are essential for analyzing AC circuits, especially involving complex quantities.
- Impedance (Z) and Admittance (Y) are vector quantities, while Conductance (G) and Susceptance (B) are scalar.
- They represent opposition or ease to current flow in AC systems.

Impedance (Z)

- Impedance is the total opposition to current in an AC circuit.
- It includes both resistance (R) and reactance (X):

$$Z = R + jX$$

- R: Resistive component
- X: Reactance (can be inductive or capacitive)
- j: Imaginary unit ($\sqrt{-1}$)

Magnitude:

$$|Z| = \sqrt{R^2 + X^2}$$

- Unit: Ohm (Ω)

Admittance (Y)

- Admittance is the reciprocal of impedance:

$$Y = 1 / Z$$

- It indicates how easily current can flow.

- Expressed as:

$$Y = G + jB$$

- G: Conductance
- B: Susceptance

Magnitude:

$$|Y| = \sqrt{G^2 + B^2}$$

- Unit: Siemens (S)

Conductance (G)

- Conductance is the real part of admittance.
- Represents the part of current that is in phase with voltage.

$$G = R / (R^2 + X^2)$$

- Unit: Siemens (S)
- In a purely resistive circuit:

$$G = 1 / R$$

Susceptance (B)

- Susceptance is the imaginary part of admittance.
- Represents the reactive component of current:

$$B = -X / (R^2 + X^2)$$

- Positive B → Capacitive
- Negative B → Inductive

In purely reactive circuits:

- For inductors: $B = -1 / X_L$
- For capacitors: $B = +1 / X_C$

Mathematical Relationships

$$Z = R + jX$$

$$Y = 1 / Z = G + jB$$

$$G = \text{Re}(Y), \quad B = \text{Im}(Y)$$

$$|Z| = 1 / |Y|$$

- Ohm's Law in AC form:

$$V = IZ$$

$$I = VY$$

Phasor Domain View

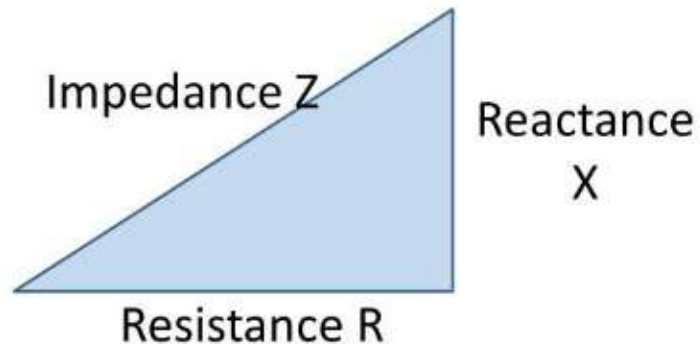


Figure 2.1 Impedance Triangle

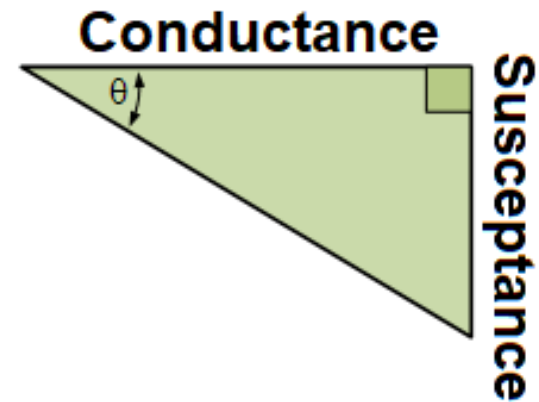


Figure 2.2 Admittance Triangle

Summary

- Impedance (Z): Opposition to AC, includes resistance and reactance.
- Admittance (Y): Ease of AC flow, reciprocal of Z .
- Conductance (G): Real part of admittance, represents resistive behavior.
- Susceptance (B): Imaginary part of admittance, represents reactive behavior.
- These terms are essential for solving and analyzing AC networks, especially in parallel circuits and phasor analysis.

Parul[®]
University

NAAC
GRADE **A++**



<https://paruluniversity.ac.in/>



Concept of Active Power, Reactive Power, Apparent Power and Power Factor

Meet Soni

Assistant Professor
Electrical Engineering

Content

1.Introduction	3
2.Active Power (P)	4
3.Reactive Power (Q)	5
4.Apparent Power (S)	6
5.Power Triangle	7
6.Power Factor (PF)	8
7.Significance of Power Factor	9
8.Key Points / Summary	10

Introduction

- In AC circuits, power is not just a product of voltage and current.
- Due to phase difference, different types of power are defined:
 1. Active Power (P)
 2. Reactive Power (Q)
 3. Apparent Power (S)
- These quantities help understand how efficiently power is utilized.

Active Power (P)

- Also known as real or true power.
- Represents the actual power consumed by resistive components.

Formula:

$$P = V \times I \times \cos(\varphi)$$

- V: RMS Voltage
 - I: RMS Current
 - ϕ : Phase angle between V and I
 - Unit: Watt (W)
-
- It performs useful work: lighting, heating, rotating machines.

Reactive Power (Q)

- Power that oscillates between source and reactive components (L and C).
- Does not perform any net work.

Formula:

$$Q = V \times I \times \sin(\varphi)$$

- Unit: VAR (Volt-Ampere Reactive)
- It supports the magnetic and electric fields in inductors and capacitors.

Apparent Power (S)

- The product of RMS voltage and current, regardless of phase angle.

Formula:

$$S = V \times I$$

- Unit: VA (Volt-Ampere)
- Represents the total power delivered to the circuit.

Relationship:

$$S^2 = P^2 + Q^2$$

Power Triangle

A right-angled triangle representing:

- Active power (P) – Base
- Reactive power (Q) – Height
- Apparent power (S) – Hypotenuse

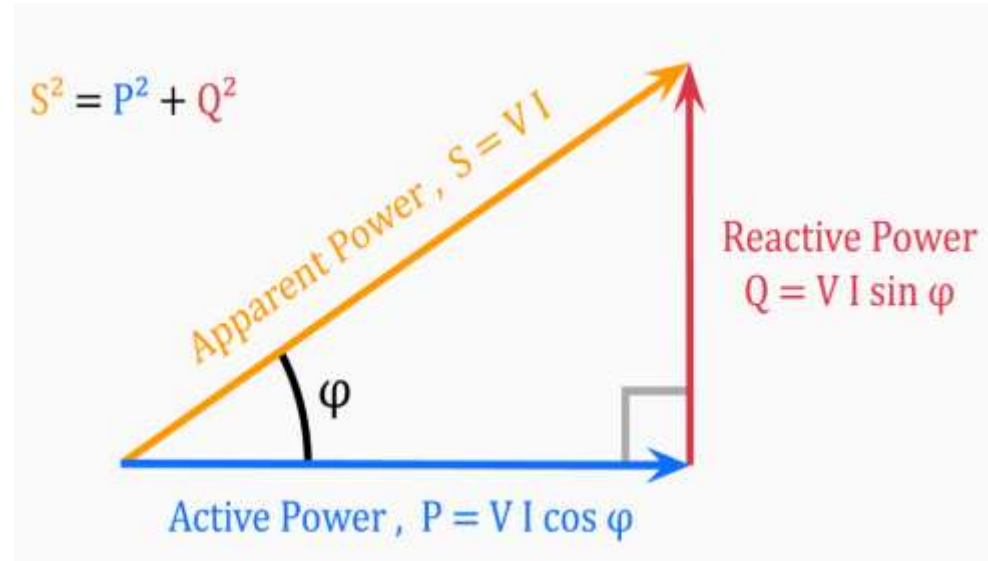


Figure 2.1 Power Triangle

Power Factor (PF)

- Indicates how effectively electrical power is converted into useful work.

Formula:

$$\text{Power Factor (PF)} = \cos(\varphi) = P / S$$

- PF ranges from 0 to 1
 - $\text{PF} = 1 \rightarrow$ purely resistive (ideal)
 - $\text{PF} < 1 \rightarrow$ reactive power is present
- Can be leading (capacitive) or lagging (inductive)

Significance of Power Factor

- Higher PF means better efficiency and reduced power losses.
- Low PF results in:
 1. Increased current
 2. Larger conductor sizes
 3. Higher losses
 4. Voltage drops
- Industries are penalized for low PF – hence power factor correction is common using capacitor banks or synchronous condensers.

Summary

- Active Power (P): Useful power consumed (W).
- Reactive Power (Q): Oscillating power (VAR).
- Apparent Power (S): Total supplied power (VA).
- Power Factor (PF): Efficiency ratio ($\cos(\phi)$).
- Power Triangle helps visualize the relationship among P, Q, and S.
- Efficient systems aim for high power factor to reduce losses and improve performance.

Parul[®]
University

NAAC
GRADE **A++**



<https://paruluniversity.ac.in/>



Concept of three phase supply and phase sequence

Meet Soni

Assistant Professor
Electrical Engineering

Content

1. Introduction to Three-Phase System	3
2. Advantages of Three-Phase Supply	4
3. Construction and Generation	5
4. Phase Sequence	6
5. Types of Connections	7
6. Significance of Phase Sequence	8
7. Applications	9
8. Key Points / Summary	10

Introduction to Three-Phase System

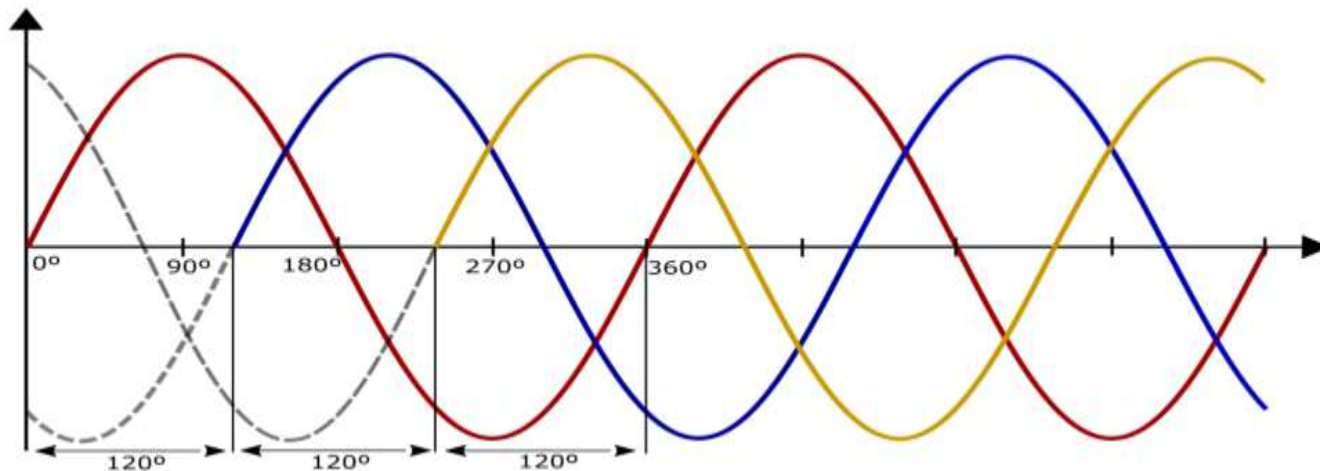


Figure 2.1 Three Phase AC supply waveform

- A three-phase system consists of three alternating voltages of the same frequency, 120° phase difference apart.
- Generated using a three-phase alternator with three windings 120° apart.
- Commonly used in industrial and power systems for efficient energy transfer.

Advantages of Three-Phase Supply

- More power delivered for the same current than single-phase.
- Constant power output – unlike pulsating power in single-phase.
- Requires less conductor material for transmission.
- Motors run more smoothly and efficiently.


Construction and Generation

- Generated by rotating a magnetic field inside a stator with three windings placed 120° apart.
- The output voltages are:
 - Balanced: Equal magnitude, 120° apart.
 - Unbalanced: Unequal magnitudes or angle deviations (not preferred).
- Voltage Equations (Balanced):
$$V_R(t) = V_m \times \sin(\omega t)$$
$$V_Y(t) = V_m \times \sin(\omega t - 120^\circ)$$
$$V_B(t) = V_m \times \sin(\omega t - 240^\circ)$$

Phase Sequence


- Phase sequence refers to the order in which the voltages attain their maximum positive values.
- In a standard system, it is either:
 1. $R \rightarrow Y \rightarrow B$ (Clockwise)
 2. $R \rightarrow B \rightarrow Y$ (Counterclockwise)
- Phase sequence is crucial in rotating machinery (e.g., motors) as it determines rotation direction.

Types of Connections

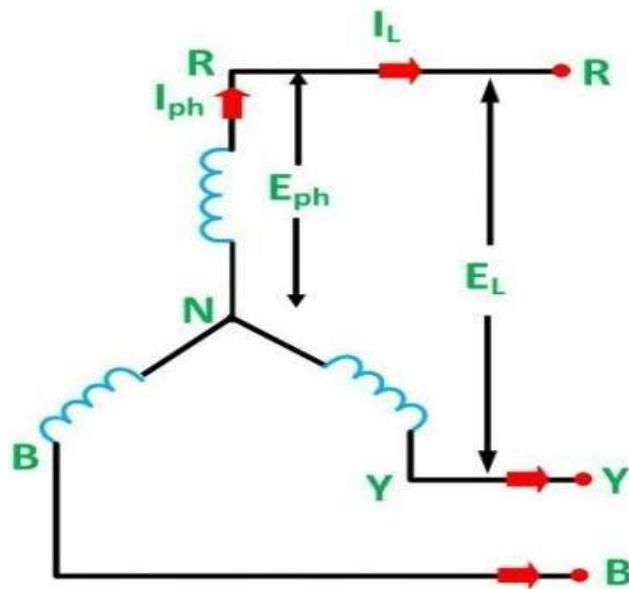

Star (Y) Connection:

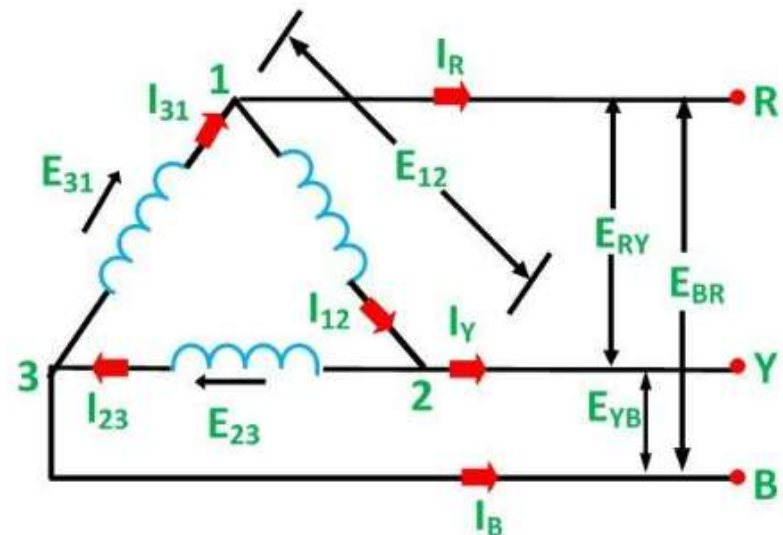- 3 phase wires + 1 neutral
- Line voltage = $\sqrt{3} \times$ Phase voltage



Delta (Δ) Connection:

- 3 phase wires only
- Line voltage = Phase voltage

Significance of Phase Sequence

Incorrect phase sequence can:

- Reverse motor direction
- Damage sensitive equipment

Critical in:

- Synchronizing alternators
- Phase-sensitive devices
- Control circuits and automation

Applications

- Power distribution systems
- Three-phase motors and generators
- Heavy industrial loads
- HVAC systems
- Electric trains and escalators

Summary

- Three-phase supply uses 3 sinusoidal voltages 120° apart.
- Delivers more power efficiently and continuously.
- Phase sequence determines the direction of rotation in motors.
- Star and Delta are two main connection types.
- Understanding sequence is vital for system protection and synchronization.

Parul[®]
University

NAAC
GRADE **A++**



<https://paruluniversity.ac.in/>

